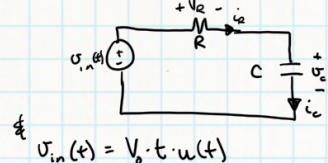


Given



$$V_{in}(t) = V_o \cdot t \cdot u(t)$$

all the $u(t)$ does it set all values of V_{in} :
for $t < 0$ then $V_{in} = 0$.

∴ we only have values for $t > 0$
 \therefore $V_{in}(t) = V_o \cdot t$
 each of a line w/ b intercept @ the origin.

Therefore to solve for the current in this problem we must 1^{st} solve the O.D.E. WRT the $V_c(t)$.

Let's make our equations:

KVL

$$V_{in} = V_R + V_C$$

KCL

$$i_m = i_R = i_C$$

time equations for $t > 0$

$$V_R = R \cdot i_R \quad \text{given: } V_{in} = V_o \cdot t$$

$$i_C = C V_C'$$

starting w/ the KVL and plugging in time domain eqn's as needed:

$$V_o \cdot t = R i_R + V_C$$

$$\therefore V_o \cdot t = R C V_C' + V_C$$

∴ the O.D.E. becomes

$$V_C' + \frac{1}{RC} V_C = \frac{V_o t}{RC}$$

Solving for homogeneous soln:

we set driving function to 0:

$$V_C' + \frac{1}{RC} V_C = 0$$

the general soln form is

$$V_{c,H}(t) = K_1 e^{\frac{s t}{RC}}$$

we solve the characteristic eqn to find, s :

$$s + \frac{1}{RC} = 0 \rightarrow s = -\frac{1}{RC}$$

$$\therefore V_{c,H}(t) = K_1 e^{-\frac{t}{RC}}$$

Solving for the particular soln:

we find a general form that is of the same form as the driving function. In this case, the driving function is a polynomial to the 1st power:

$$\therefore V_{c,P}(t) = A \cdot t + B \quad \text{and } V_C'(t) = A$$

plugging this back into the O.D.E. we get:

$$\underbrace{(A)}_{V_C'} + \underbrace{\left(\frac{A+t+B}{RC}\right)}_{V_C} = \frac{V_o \cdot t}{RC}$$

Rearranging we get:

$$\underbrace{\left(\frac{A}{RC}\right)t + \left(\frac{B}{RC} + A\right)}_{(A \cdot t + B)} = \underbrace{\left(\frac{V_o}{RC}\right)t + 0}_{V_o \cdot t}$$

we see for these 2 eqn to be equal, then

$$\frac{A}{RC} = \frac{V_o}{RC} \quad \& \quad \frac{B}{RC} + A = 0$$

↓

$$\therefore A = V_o \quad \& \quad B = -ARC = -V_o RC$$

∴ the particular soln becomes

$$V_{c,P}(t) = A \cdot t + B = V_o \cdot t - V_o RC$$

and the general solution becomes

for $t > 0$

$$V_C(t) = V_{c,H}(t) + V_{c,P}(t)$$

$$V_C(t) = K_1 e^{-\frac{t}{RC}} + V_o \cdot t - V_o RC$$

if we make $\tau = RC$

we get

$$V_C(t) = K_1 e^{-\frac{t}{\tau}} + (t - \tau) V_o$$

using our ic. we get

$$V_C(0) = 0 = K_1 e^0 + (0 - \tau) V_o$$

$$\therefore K_1 = V_o \tau$$

and the solution becomes:

$$V_C(t) = V_o \tau e^{-\frac{t}{\tau}} + V_o t - V_o \tau$$

to find i we can find i_c . This is $i_c = C V_C'$

∴ for $t > 0$:

$$i(t) = C \left[-V_o e^{-\frac{t}{\tau}} + V_o \right] = V_o C \left[1 - e^{-\frac{t}{\tau}} \right]$$

if we integrate the input because this is a LTI system the answer should be integrated.
 \therefore if the input is

$$\int V_o t dt = \frac{V_o t^2}{2} + C_1$$

$$\therefore V_P = \int V_o \tau e^{-\frac{t}{\tau}} + V_o t - V_o \tau dt$$

$$= -V_o \tau^2 e^{-\frac{t}{\tau}} + \frac{V_o t^2}{2} - V_o \tau t + C_2$$

$$\text{if } V_o \cos 0 \text{ then } C_2 = V_o \tau^2$$

$$\therefore V_C(t) = -V_o \tau^2 e^{-\frac{t}{\tau}} + \frac{V_o t^2}{2} - V_o \tau \cdot t + V_o \tau^2$$

$$\text{Check this: } V_{in} = \frac{V_o t^2}{2}$$

$$\text{Homogeneous solution is still the same}$$

$$V_{c,H}(t) = K_1 e^{-\frac{t}{\tau}}$$

$$V_{c,P}(t) = At^2 + Bt + C \quad \& \quad V_C'(t) = 2At + B$$

$$\therefore (2At + B) + \frac{(At^2 + Bt + C)}{\tau} = \frac{V_o t^2}{2\tau}$$

$$\left(\frac{A}{\tau} \right) t^2 + \left(2A + \frac{B}{\tau} \right) t + \left(B + \frac{C}{\tau} \right) = \left(\frac{V_o}{2\tau} \right) t^2 + 0 + 0$$

$$\frac{A}{\tau} = \frac{V_o}{2\tau} \quad \& \quad 2A + \frac{B}{\tau} = 0 \quad \& \quad B + \frac{C}{\tau} = 0$$

$$A = \frac{V_o}{2} \quad B = -2\tau A \quad C = -\tau B$$

$$B = -2\tau \frac{V_o}{2} \quad C = -\tau (-2\tau V_o)$$

$$B = -\tau V_o \quad C = \tau^2 V_o$$

∴ The general solution becomes:

$$V_C(t) = K_1 e^{-\frac{t}{\tau}} + \frac{V_o t^2}{2} + (-\tau V_o) t + \tau^2 V_o$$

using the ic. $V_C(0) = 0$

we get:

$$0 = K_1 e^0 + \frac{V_o (0)^2}{2} - \tau V_o (0) + \tau^2 V_o$$

$$\therefore K_1 = -\tau^2 V_o$$

and the solution becomes:

$$V_C(t) = \tau^2 V_o e^{-\frac{t}{\tau}} + \frac{V_o t^2}{2} - \tau V_o t + \tau^2 V_o$$

so we see w/ LTI systems the linear part allows us to take an already known solution and if we do something to the input we do the same to the o/p and find a new solution. something linear is like multiplication/division/integration/derivatives.

No need to go through the whole process twice once you prove this to yourself when this works.