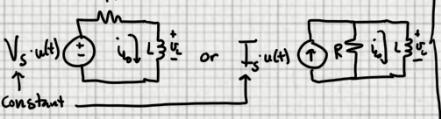


The following are equations for simple RL, RC, & RLC ckt's. They take into account initial conditions. These are for DC driven ckt's that have a turn on time of $t=0$. Therefore, $t \geq 0$ for $V_s(t)$ & $i_L(t)$.

Given: $V_s(t)$ where: $i_L(0) = i_{L0}$



we know the O.D.E. is

$$i_L' + \frac{R}{L} i_L = \frac{V_s}{L} \quad \text{where } I_s = \frac{V_s}{R}$$

The Homogeneous Solution:

$$i_{LH} = K_1 e^{st}$$

where the characteristic eqn is:

$$s + \frac{R}{L} = 0 \rightarrow s = -\frac{R}{L}$$

$$\therefore i_{LH} = K_1 e^{-\frac{Rt}{L}}$$

The Particular Solution:

i_{LP} will be of the form of the driving function.

Since the driving function is constant then so will i_{LP} .

$$i_{LP} = A \quad \text{and} \quad i_{LP}' = 0$$

Plugging back into equation

$$0 + \frac{R}{L} \cdot A = \frac{R}{L} I_s \quad \therefore A = I_s$$

General Solution:

$$i_L(t) = K_1 e^{-\frac{Rt}{L}} + I_s$$

using initial condition:

$$i_L(0) = i_{L0} = K_1 + I_s$$

$$\therefore K_1 = (i_{L0} - I_s)$$

$$\therefore i_L(t) = (i_{L0} - I_s) e^{-\frac{Rt}{L}} + I_s \quad \text{for } t \geq 0$$

$$\text{given } V_L(t) = L i_L'(t)$$

$$V_L(t) = -R(i_{L0} - I_s)e^{-\frac{Rt}{L}}$$

Remember you don't want:




because @ steady state the inductor becomes a wire and the current goes to infinity



because @ $t=0$ the current of the inductor is being forced to instantaneously go from 0 to some value. The voltage across it would have to be infinite

Given:
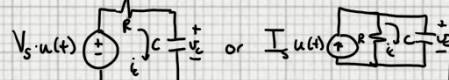
$$V_s(t) \quad \text{where } V_s(0) = V_{s0}$$



we know the O.D.E.

$$V_C' + \frac{1}{RC} V_C = \frac{V_s}{RC} \quad \text{where } V_s = R \cdot I_s$$

Homogeneous Solution:

$$V_{CH} = K_1 e^{-\frac{t}{RC}}$$

Particular Solution:

$$V_{CP} = V_s$$

General Solution

$$V_C(t) = K_1 e^{-\frac{t}{RC}} + V_s$$

using i.c.


$$V_C(0) = V_{C0} = K_1 + V_s \rightarrow K_1 = (V_{C0} - V_s)$$

$$\therefore V_C(t) = (V_{C0} - V_s) e^{-\frac{t}{RC}} + V_s \quad \text{for } t \geq 0$$


$$\text{since } i_C(t) = C V_C'(t)$$

$$i_C(t) = -\frac{(V_{C0} - V_s)}{R} e^{-\frac{t}{RC}}$$

Remember you Don't want:

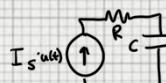


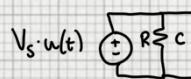because the current source will always be charging up the capacitor and the voltage across it will go to infinity



because @ $t=0$ the voltage across the capacitor jumps instantaneously from 0 to some value. The current going to the capacitor would have to infinite.

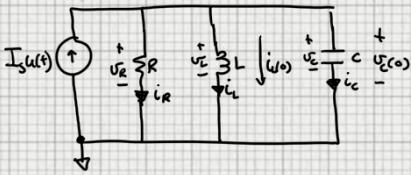RLC parallel
ckt analysis of DC
current input w/ initial
conditions.



Given for $t \geq 0$,

Driving function is DC current w/ value of "I_s"

$$\text{and } i_s(t) = i_o \quad \& \quad v_c(t) = v_{co}$$

We know the O.D.E. is

$$i'' + \frac{1}{RC} i' + \frac{1}{LC} i = \frac{I_s}{LC}$$

We also know the particular solution is set by the driving function, so its form does not change w/ R, L, or C

Solving for Particular Solution we find i_{sp} is of the same form as the driving function; constant.

$$\therefore i_{sp} = A \quad \& \quad i_{sp}' = i_{sp}'' = 0$$

$$\therefore 0 + \frac{1}{RC} \cdot 0 + \frac{1}{LC} \cdot A = \frac{I_s}{LC} \rightarrow A = I_s$$

$$\therefore i_{sp} = I_s$$

Now solving for the 3 cases of the homogeneous solution. Before starting let's define some terms.

σ , damping coefficient, ($\frac{1}{s}$)

ω_n , natural frequency, ($\frac{rad}{s}$)

ω_d , damped frequency, ($\frac{rad}{s}$)

ζ , raper frequency, (unitless)

general forms of Homogeneous solutions

$$1) \text{ overclamped when } \sigma^2 > \omega_n^2 \\ i_{ht1} = K_1 e^{-\zeta \sqrt{\sigma^2 - \omega_n^2} t} + K_2 e^{-(\sigma + \zeta \sqrt{\sigma^2 - \omega_n^2}) t}$$

$$2) \text{ critically damped when } \sigma^2 = \omega_n^2 \\ i_{ht2} = (K_1 + K_2 t) e^{-\sigma t}$$

$$3) \text{ underdamped when } \sigma^2 < \omega_n^2 \\ i_{ht3} = e^{-\sigma t} [K_1 \cos(\omega_d t) + K_2 \sin(\omega_d t)]$$

what is ω_d , damped frequency?

it is an oscillation of the system that oscillates slower than the natural frequency.

The form is given by:

$$\omega_d = \omega_n \sqrt{1 - \frac{\sigma^2}{\omega_n^2}}$$

since the raper ratio is

$$\zeta = \frac{\sigma}{\omega_n}$$

$$\omega_d = \omega_n \sqrt{1 - \zeta^2}$$

note: ζ must be less than 1

Therefore, the 3 general Solutions are:

$$1) K_1 e^{-\frac{(\sigma - \sqrt{\sigma^2 - \omega_n^2})t}{\Delta}} + K_2 e^{-\frac{(\sigma + \sqrt{\sigma^2 - \omega_n^2})t}{\Delta}} + I_s$$

$$2) e^{-\sigma t} (K_1 + K_2 t) + I_s$$

$$3) e^{-\sigma t} [K_1 \cos(\omega_d t) + K_2 \sin(\omega_d t)]$$

Let's solve using i.c.

$$1) i_{o(0)} = i_{o0} = K_1 + K_2 + I_s \rightarrow K_1 = i_{o0} - (K_2 + I_s)$$

$$\text{since } v_c = v_L = L i_L'$$

$$v_{co}(0) = v_{co} = L [K_1 (\Delta) + K_2 (-\star)]$$

$$\therefore \frac{v_{co}}{L} = (-i_{o0} + K_2 + I_s) \Delta - K_2 \star$$

$$\therefore K_2 (\Delta - \star) = \frac{v_{co}}{L} + \Delta (i_{o0} - I_s)$$

$$\therefore K_2 = \frac{v_{co} + \Delta L (i_{o0} - I_s)}{L (\Delta - \star)}$$

$$K_1 = (i_{o0} - I_s) - \frac{v_{co} + \Delta L (i_{o0} - I_s)}{L (\Delta - \star)}$$

$$K_1 = \frac{\Delta L (i_{o0} - I_s) - \star L (i_{o0} - I_s) - v_{co} - \Delta L (i_{o0} - I_s)}{L (\Delta - \star)}$$

$$K_1 = -\frac{(v_{co} + \star L (i_{o0} - I_s))}{L (\Delta - \star)}$$

\therefore for case 1:

$$i_{ht1}(t) = -\frac{(v_{co} + \star L (i_{o0} - I_s))}{L (\Delta - \star)} e^{-\Delta t} + \frac{(v_{co} + \Delta L (i_{o0} - I_s))}{L (\Delta - \star)} e^{\star t} + I_s$$

where

$$\Delta = \sigma - \sqrt{\sigma^2 - \omega_n^2} \quad \& \quad \star = \sigma + \sqrt{\sigma^2 - \omega_n^2}$$

$$\sigma = \frac{1}{2RC} \quad \omega_n^2 = \frac{1}{LC}$$

For Case 2, critically damped

$$\sigma^2 = \omega_n^2$$

$$\text{then: } i_{ht2} = e^{-\sigma t} (K_1 + K_2 t) + I_s$$

$$\therefore i_{ht2}(0) = i_{o0} = K_1 + I_s$$

$$K_1 = i_{o0} - I_s$$

$$\text{again } v_c = v_L = L i_L'$$

$$\frac{v_{co}(0)}{L} = \frac{v_{co}}{L} = -\sigma K_1 + K_2$$

$$K_2 = \frac{v_{co}}{L} + \sigma (i_{o0} - I_s)$$

$$\therefore \text{for case 2 } \frac{\sigma^2}{\omega_n^2} = \frac{(\frac{1}{2RC})^2}{\frac{1}{LC}} = \frac{1}{4}$$

$$i_{ht2}(t) = e^{-\sigma t} [i_{o0} - I_s + t \left(\frac{v_{co} + \sigma L (i_{o0} - I_s)}{L} \right)] + I_s$$

$$\text{where } \sigma = \frac{1}{2RC}$$

For case 3, underdamped

$$i_{ht3}(t) = e^{-\sigma t} [K_1 \cos(\omega_d t) + K_2 \sin(\omega_d t)] + I_s$$

$$i_{o3}(0) = i_{o0} = K_1 + I_s \rightarrow K_1 = i_{o0} - I_s$$


$$\therefore K_2 = \frac{v_{co} + \sigma L (i_{o0} - I_s)}{\omega_d L}$$

$$\therefore \text{for case 3 } \sigma^2 < \omega_n^2 \quad \left(\frac{1}{2RC} \right)^2 < \frac{1}{LC}$$

$$i_{ht3}(t) = e^{-\sigma t} [(i_{o0} - I_s) \cos(\omega_d t) + \dots \left(\frac{v_{co} + \sigma L (i_{o0} - I_s)}{\omega_d L} \right) \sin(\omega_d t)] + I_s$$

$$\text{where } \sigma = \frac{1}{2RC} \quad \omega_d = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{(\frac{1}{2RC})^2}{\frac{1}{LC}}}$$

If given:

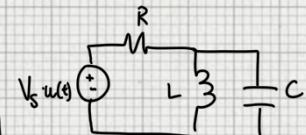


The same equations apply. The only consideration is the source transform where

$$I_s = \frac{V_s}{R}$$

just replace and go

Given the ckt:

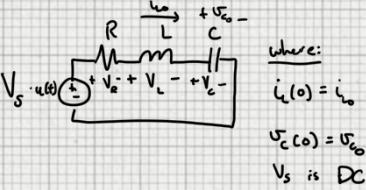

we know the ODE is:

$$\frac{V_C''}{2\sigma} + \frac{R}{L} V_C' + \frac{1}{LC} V_C = \frac{V_s}{LC}$$

we know the particular solution must be of the same form as the driving function:

$$\therefore V_{cp} = A \quad \& \quad V_{cp}' = V_{cp}'' = 0$$

plugging back in we get:

$$0 + \frac{R}{L} \cdot 0 + \frac{A}{LC} = \frac{V_s}{LC} \therefore A = V_s$$

$$\therefore V_{cp} = V_s$$

Homogeneous solution has 3 cases:

$$1) \sigma^2 > \omega_n^2$$

$$\therefore V_{ch1} = K_1 e^{-\sigma t} + K_2 e^{-\sigma t}$$

$$2) \sigma^2 = \omega_n^2$$

$$\therefore V_{ch2} = e^{-\sigma t} (K_1 + K_2 t)$$

$$3) \sigma^2 < \omega_n^2$$

$$\therefore V_{ch3} = e^{-\sigma t} (K_1 \cos(\omega_d t) + K_2 \sin(\omega_d t))$$

where:

$$\sigma = \text{damping coefficient} = \frac{1}{2RC}$$

$$\omega_n = \text{natural frequency} = \frac{1}{LC}$$

$$\omega_d = \text{damped frequency} = \omega_n \sqrt{1 - \zeta^2}$$

$$\zeta = \text{rever frequency} = \frac{\sigma}{\omega_n}$$

↳ where $0 < \zeta < 1$

$$\therefore \omega_d = \frac{1}{LC} \sqrt{1 - \frac{1}{4\sigma^2}}$$

Recall we just set:

$$\Delta = \sigma - \sqrt{\sigma^2 - \omega_n^2} \quad \& \quad \star = \sigma + \sqrt{\sigma^2 - \omega_n^2}$$

Case 1 solution

$$V_C(t) = K_1 e^{-\sigma t} + K_2 e^{-\sigma t} + V_s$$

$$V_C(0) = V_{C0} = K_1 + K_2 + V_s \rightarrow K_1 = V_{C0} - K_2$$

$$\text{since } i_L = i_C = C V_C' \quad \therefore K_2 = V_C -$$

$$\frac{i_L(t)}{C} = -K_1 \Delta e^{-\sigma t} - K_2 \star e^{-\sigma t}$$

$$\frac{i_L(0)}{C} = \frac{i_{L0}}{C} = -K_1 \Delta - K_2 \star$$

$$\therefore \frac{i_{L0}}{C} = -(V_{C0} - (K_2 + V_s)) \Delta - \star K_2$$

$$K_2 = \left(\frac{i_{L0}}{C} + (V_C - V_s \Delta) \right) / (\Delta - \star)$$

$$\therefore K_2 = \frac{i_{L0}}{C} + \frac{(V_{C0} - V_s) \Delta}{(\Delta - \star)}$$

$$K_2 = \frac{i_{L0} + \Delta C (V_{C0} - V_s)}{C (\Delta - \star)}$$

$$K_1 = (V_{C0} - V_s) - \left(\frac{i_{L0} + \Delta C (V_{C0} - V_s)}{C (\Delta - \star)} \right)$$

$$K_1 = \frac{\Delta C (V_{C0} - V_s) - \star C (V_C - V_s) - i_{L0} - \Delta C (V_C - V_s)}{C (\Delta - \star)}$$

$$K_1 = - \frac{(i_{L0} + \star C (V_C - V_s))}{C (\Delta - \star)}$$

for Case 1 $\sigma^2 > \omega_n^2$

$$V_C(t) = - \frac{(i_{L0} + \star C (V_{C0} - V_s))}{C (\Delta - \star)} e^{-\Delta t} + \dots$$

$$\dots \frac{(i_{L0} + \Delta C (V_{C0} - V_s))}{C (\Delta - \star)} e^{-\star t} + V_s$$

For Case 2 $\sigma^2 = \omega_n^2$

$$V_C(t) = e^{-\sigma t} (K_1 + K_2 t) + V_s$$

$$V_C(0) = V_{C0} = K_1 + V_s \rightarrow K_1 = V_{C0} - V_s$$

$$\text{using } i_L = i_C = C V_C'$$

$$\frac{i_L(t)}{C} = -\sigma e^{-\sigma t} (K_1 + K_2 t) + e^{-\sigma t} (K_2)$$

$$\frac{i_L(0)}{C} = \frac{i_{L0}}{C} = -\sigma K_1 + K_2$$

$$\therefore K_2 = \frac{i_{L0}}{C} + \sigma (V_{C0} - V_s)$$

for Case 2 $\sigma^2 = \omega_n^2$

$$V_C(t) = e^{-\sigma t} [(V_{C0} - V_s) + \left(\frac{i_{L0}}{C} + \sigma (V_{C0} - V_s) \right) t] + V_s$$

For Case 3 $\sigma^2 < \omega_n^2$

$$V_C(t) = e^{-\sigma t} [K_1 \cos(\omega_d t) + K_2 \sin(\omega_d t)] + V_s$$

$$V_C(0) = V_{C0} = K_1 + V_s \rightarrow K_1 = V_{C0} - V_s$$

$$\frac{i_L(t)}{C} = e^{-\sigma t} [-K_1 \omega_d \sin(\omega_d t) + K_2 \omega_d \cos(\omega_d t)] \dots$$

$$\dots -\sigma e^{-\sigma t} [K_1 \cos(\omega_d t) + K_2 \sin(\omega_d t)]$$

$$\frac{i_L(0)}{C} = \frac{i_{L0}}{C} = K_2 \omega_d - \sigma K_1$$


$$\therefore K_2 = \frac{i_{L0}}{\omega_d C} + \frac{\sigma (V_{C0} - V_s)}{\omega_d}$$

for Case 3 $\sigma^2 < \omega_n^2$

$$V_C(t) = e^{-\sigma t} [(V_{C0} - V_s) \cos(\omega_d t) + \left(\frac{i_{L0}}{\omega_d C} + \frac{\sigma (V_{C0} - V_s)}{\omega_d} \right) \sin(\omega_d t)] + V_s$$

Note:

the same equations apply for the ckt.

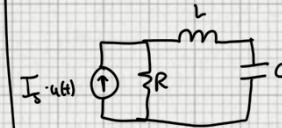


The source transformation yields

$$V_s = I_s \cdot R$$

Quick Reference

Given

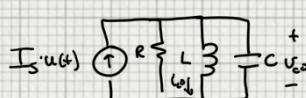

The O.D.E. is:

$$i'' + \frac{1}{RC} i' + \frac{1}{LC} i = \frac{I_s}{LC} = \frac{V_s}{RLC}$$

$$\sigma = \frac{1}{2RC} \quad \omega_n = \frac{1}{\sqrt{LC}} \quad \omega_d = \sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}}$$

where: $0 < \frac{1}{4R^2C^2} < 1$

$$\star - \Delta = 2\sqrt{\left(\frac{1}{2\omega_n}\right)^2 - \frac{1}{\omega_d^2}}$$

$$\Delta = \frac{1}{2RC} - \sqrt{\left(\frac{1}{2\omega_n}\right)^2 - \frac{1}{\omega_d^2}} \quad \star = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2\omega_n}\right)^2 - \frac{1}{\omega_d^2}}$$

$$\star \cdot \Delta = \frac{1}{LC}$$

Case 1 $\sigma^2 > \omega_n^2$

$$i_o(t) = \frac{v_{c0} + \star L(i_o - I_s)}{L(\star - \Delta)} e^{-\star t} - \frac{v_{c0} + \Delta L(i_o - I_s)}{L(\star - \Delta)} e^{-\Delta t} + I_s$$

$$v_c(t) = - \left(\frac{\Delta L v_{c0} + \frac{1}{C} (i_o - I_s)}{\star - \Delta} \right) e^{-\Delta t} + \left(\frac{\star v_{c0} + \frac{1}{C} (i_o - I_s)}{\star - \Delta} \right) e^{-\star t}$$

Case 2 $\sigma^2 = \omega_n^2$

$$i_o(t) = e^{-\frac{t}{2RC}} \left[(i_{o0} - I_s) + \left(\frac{v_{c0}}{L} + \frac{1}{2RC} (i_{o0} - I_s) \right) \cdot t \right] + I_s$$


$$v_c(t) = \frac{L}{2RC} e^{-\frac{t}{2RC}} \left[\frac{2RC}{L} v_{c0} - \left(\frac{v_{c0}}{L} + \frac{1}{2RC} (i_{o0} - I_s) \right) \cdot t \right]$$

Case 3 $\sigma^2 < \omega_n^2$

$$i_o(t) = e^{-\frac{t}{2RC}} \left[(i_{o0} - I_s) \cos(\omega_d t) + \left(\frac{v_{c0}}{w_n L} + \frac{(i_{o0} - I_s)}{2w_n RC} \right) \sin(\omega_d t) \right] + I_s$$

$$v_c(t) = e^{-\frac{t}{2RC}} \left[v_{c0} \cos(\omega_d t) - \frac{L}{2RC} \left(\frac{v_{c0}}{w_n L} + \frac{(i_{o0} - I_s)}{2w_n RC} \right) + 2w_n RC (i_{o0} - I_s) \right] \sin(\omega_d t)$$

Given:

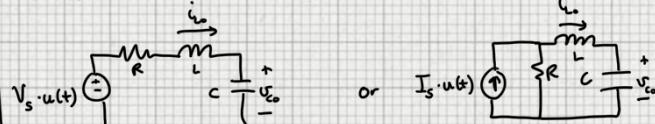

The O.D.E. is:

$$i'' + \frac{R}{LC} i' + \frac{1}{LC} i = \frac{V_s}{LC} = \frac{R}{LC} \cdot I_s$$

$$\sigma = \frac{R}{2LC} \quad \omega_n = \frac{1}{\sqrt{LC}} \quad \therefore \omega_n^2 = \frac{1}{LC}$$

$$\zeta^2 = \frac{\sqrt{LC} \cdot R}{2LC} \quad \therefore \zeta^2 = \frac{R^2 C}{4LC} \quad \rightarrow \omega_d = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{R^2 C}{4LC}}$$

where: $0 < \frac{R^2 C}{4LC} < 1$

$$\Delta = \frac{R}{2LC} - \sqrt{\left(\frac{R}{2\omega_n}\right)^2 - \frac{1}{\omega_d^2}}$$

$$\star = \frac{R}{2LC} + \sqrt{\left(\frac{R}{2\omega_n}\right)^2 - \frac{1}{\omega_d^2}}$$

$$\Delta \cdot \star = \frac{1}{LC}$$

$$\star - \Delta = 2\sqrt{\left(\frac{R}{2\omega_n}\right)^2 - \frac{1}{\omega_d^2}}$$

Case 1 $\sigma^2 > \omega_n^2$

$$v_c(t) = \frac{i_{o0} + \star C(v_c - V_s)}{C(\star - \Delta)} e^{-\star t} - \frac{i_{o0} + \Delta C(v_c - V_s)}{C(\star - \Delta)} e^{-\Delta t} + V_s$$

$$i_o(t) = - \left(\frac{i_{o0} + \frac{1}{C}(v_{c0} - V_s)}{\star - \Delta} \right) e^{-\Delta t} + \left(\frac{\star i_{o0} + \frac{1}{C}(v_{c0} - V_s)}{\star - \Delta} \right) e^{-\star t}$$

Case 2 $\sigma^2 = \omega_n^2$

$$v_c(t) = e^{-\frac{R}{2LC} t} \left[(v_{c0} - V_s) + \left(\frac{i_{o0}}{C} + \frac{R}{2LC} (v_{c0} - V_s) \right) \cdot t \right] + V_s$$

$$i_o(t) = \left(\frac{RC}{2L} \right) e^{-\frac{R}{2LC} t} \left[\frac{2L}{RC} i_{o0} - \left(\frac{i_{o0}}{C} + \frac{R}{2LC} (v_{c0} - V_s) \right) \cdot t \right]$$


Case 3 $\sigma^2 < \omega_n^2$

$$v_c(t) = e^{-\frac{R}{2LC} t} \left[(v_{c0} - V_s) \cos(\omega_d t) + \left(\frac{i_{o0}}{w_n C} + \frac{R(v_{c0} - V_s)}{2w_n LC} \right) \sin(\omega_d t) \right] + V_s$$


$$i_o(t) = e^{-\frac{R}{2LC} t} \left[i_{o0} \cos(\omega_d t) - \frac{RC}{2LC} \left(\frac{i_{o0}}{w_n C} + \frac{R(v_{c0} - V_s)}{2w_n LC} \right) + \frac{2w_n L(v_{c0} - V_s)}{R} \sin(\omega_d t) \right]$$

These solutions are for $t \geq 0$ for simple RLC ckt's driven by DC sources that turn on @ $t=0$. Initial conditions need to be found or given.

Over damped

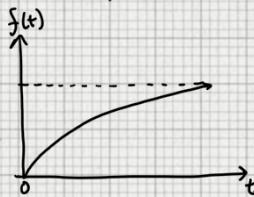

Critically Damped

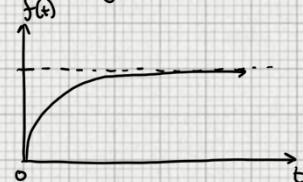

Under damped

