
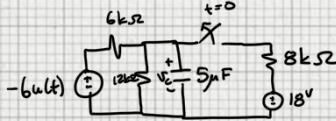


Given the ckt:

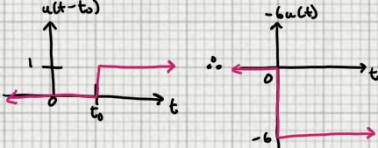


The unit step function (Heaviside) function is a piecewise function given by:

$$u(t-t_0) = \begin{cases} 1, & \text{arg}(t) \geq 0, t-t_0 \geq 0 \Rightarrow t \geq t_0 \\ 0, & \text{otherwise} \end{cases}$$



Assuming the switch is closed for a long time what is $V_C(t)$ when $t=0^+$.

Well the ckt @ $t=0^-$ is:

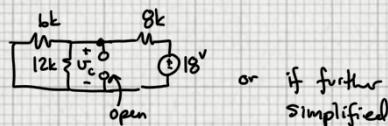

or if further simplified

$$18V \xrightarrow{\text{parallel}} \frac{6 \cdot 12}{(6+12)} k = \frac{32}{18} k = 4k$$


Since $8k \neq 4k$ share the same current we can use the voltage divider equation.

$$V_{R_2} = \left(\frac{4k}{4k+8k} \right) 18V = 6V$$

we see that given the configuration V_{R_2} is in parallel with V_C . Therefore $V_C(t=0^-) = 6V$. Since we assume voltage cannot change instantaneously across a capacitor then

$$V_C(t=0^+) = V_C(t=0^-) = 6V$$

Given the ckt:

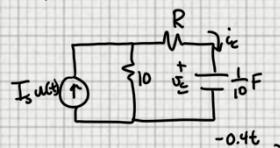


$$\left. \begin{aligned} V_C(t) &= 20 - 10e^{-0.4t} \\ i_C(t) &= 0.4e^{-0.4t} \end{aligned} \right\} \text{for } t \geq 0$$

Find the value of R.


This problem is doing nothing more than finding equivalent resistance felt by the capacitor.

Recall that any simple RC ckt has a $\tau = RC$.

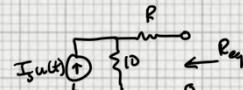We know the capacitance, we just need to find the equivalent resistance seen by capacitor. In other words:



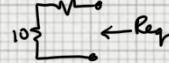When you have access to the sources, zero them out. Recall a current source with 0^A is like an open. So the ckt reduces to:



$$\therefore R_{eq} = R + 10 \Rightarrow \tau = (R + 10) \cdot 10$$

We can see from the general equation describing the voltage of a capacitor for a simple RC network:

$$V_C(t) = (V_0 - V_\infty)e^{-\frac{(t-t_0)}{\tau}} + V_\infty$$


we see that $\frac{1}{\tau} = 0.4 = \frac{1}{10}$

$$\therefore \tau = \frac{10}{4} \text{ so we equate them.}$$

$$(R + 10) \cdot \frac{1}{10} = \frac{10}{4} \rightarrow 4R + 40 = 100$$


$$\therefore 4R = 60 \rightarrow R = 15\Omega$$

Given the ckt:

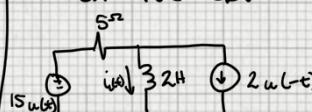


find the equation of $i_L(t)$ for $t \geq 0$.

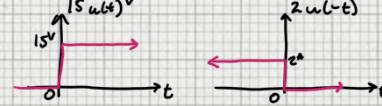The equations for the voltage & current sources look as such



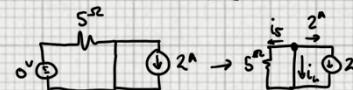we can now assume any initial states. Assuming the ckt is steady state @ negative infinity the ckt looks like



recall ohms law for resistors.


$$i_R = \frac{\Delta V_R}{R}, \text{ and since a wire drops/gains } 0^V \Delta V_R = 0^V. \text{ Due to Ohm's law } 0^V \text{ can flow}$$

through the 5Ω . So using KCL $i_5 + i_2 + 2^A = 0^A$, we see $i_2 = -2^A$.

$$\text{Our } i_0 = -2^A \quad i_L(t=0^-) = -2^A = i_L(t=0^+)$$

Since we assume current in an inductor cannot change instantaneously.

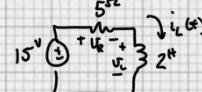Given the initial condition we can now look @ the ckt for $t \geq 0$. Which looks like:



KVL

$$15V = V_R + V_L \quad I_R = I_L$$

KCL

$$\Delta V_R = R \cdot I_R \quad \Delta V_L = L \frac{dI_L}{dt}$$

given the KCL:

$$\Delta V_R = R \cdot I_L$$

$$15 = R \cdot I_L + L I_L'$$

$$\text{or} \quad I_L' + \frac{L}{R} I_L = \frac{15}{R} \rightarrow I_L' + 2.5 I_L = 7.5$$

Homogeneous Solution

$$I_{L,H}^{(0)} = C_1 e^{-2.5t}, \text{ where the characteristic eqn: } s + 2.5 = 0 \rightarrow s = -2.5$$

Particular Solution

$$I_{L,P} = A \quad \& \quad I_{L,P}' = 0$$

$$\therefore 0 + 2.5A = 7.5$$

$$\therefore A = \frac{7.5}{2.5} = 3$$

Since the driving function is a constant we assume the particular solution is a constant.

The general solution becomes:

$$I_L(t) = I_{L,H}^{(0)} + I_{L,P}(t) = C_1 e^{-2.5t} + 3$$

Given the initial condition $I_L(t=0^+)$ we can solve for C_1 .

$$I_L(0) = -2 = C_1 e^{0} + 3 \therefore C_1 = -5$$

and the solution becomes:

$$I_L(t) = -5e^{-2.5t} + 3$$

if we use the general current equation for an inductor in a simple LR ckt we know $\tau = \frac{L}{R} = \frac{2}{5} = \frac{1}{2.5} = 0.4$

we know $t_0 = 0$

we know $I_L(0^-) = -2^A \quad I_L(\infty) = \frac{V}{R} = \frac{15}{5} = 3^A$


Plugging these values into the general equation:

$$I_L(t) = (I_{L,0} - I_{L,\infty})e^{-\frac{(t-t_0)}{\tau}} + I_{L,\infty}$$


yields the same answer but way faster. $-2.5t$

$$I_L(t) = (-2 - 3)e^{-2.5t} + 3$$

Given the ckt:

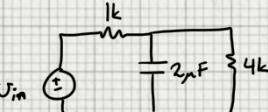
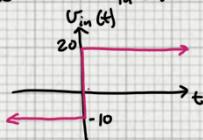
$$\text{where } V_{in}(t) = -10u(-t) + 20u(t)$$



Find the zero input response and the zero state response for $t \geq 0$.

All this is asking is,


① How does this ckt respond if the capacitor has only initial conditions and the source is zeroed out?
(zero input response) \leftarrow similar to homogeneous solution

② How does this ckt respond if the capacitor has no initial conditions and the source is the only thing exciting it?

(zero state response) \leftarrow kind of like looking \leftarrow a particular solution

Let's start w/ ①

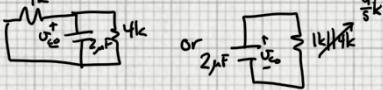if this ckt had a zeroed out source it would reduce down to



we need to find $V_c(t=0^-)$ to use as an initial condition.

@ $t = -\infty$ the capacitor acts as an open and $V_c = V_{4k}$. Using the voltage we see $V_{4k} = \frac{4}{5}V_{in}$.

$$\therefore V_c(t=0^-) = -8V \Rightarrow V_{c0} = -8V$$

with a potential of $-8V$

we see the RC network will decay to $0V$ with nothing driving it. Using the general equation

$$V_c(t) = (V_{c0} - V_{c\infty})e^{-\frac{t-t_0}{RC}} + V_{c\infty}$$

we know for this configuration

$$R = \frac{1}{2nF} = 2 \times 10^6 F$$

$$C = \frac{1}{2} \times 10^3 = 625 \mu F$$

$$t_0 = 0 \quad V_{c0} = -8V \quad V_{c\infty} = 0V$$

\therefore The zero input response is

$$V_{c,zi} = -8e^{-625t}$$

The zero state response

looks at what happens when $V_{c0} = 0V$ and $V_{in}(t=0)$

The ckt for $t \geq 0$ w/ the input becomes



τ & $\frac{1}{\tau}$ is the same.

t_0 is the same

$$V_{c0} = 0V \quad \& \quad V_{c\infty} = 20V$$

using the general voltage equation for a simple RC network

$$V_c(t) = (V_{c0} - V_{c\infty})e^{-\frac{(t-t_0)}{\tau}} + V_{c\infty}$$


\therefore

$$V_{c,zsr}(t) = (0 - 20)e^{-625t} + 20$$


or

$$V_{c,zsr}(t) = 20(1 - e^{-625t})$$

Given the ckt:

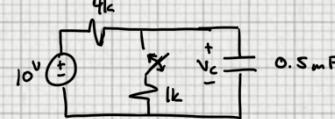

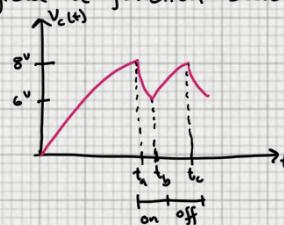Assume, $V_c(t=0) = 0V$. Also that the switch closes when $V_c = 8V$ and opens when $V_c = 6V$, to yield a function such as:



the function is given by the piecewise:

$$V_c(t) = \begin{cases} 10(1 - e^{-0.5t}), & 0 < t < t_a \text{ off} \\ 2 + 6e^{-2.5(t-t_a)}, & t_a < t < t_b \text{ on} \\ 10 - 4e^{-0.5(t-t_b)}, & t_b < t < t_c \text{ off} \\ \vdots \end{cases}$$

Find $t_b - t_a$.

You could go through multiple steps to find $t_b - t_a$ or you can literally find the time it takes for voltage to fall from $8V$ to $6V$ using the second equation in the piecewise.

Using $V_{c,out}(t) = 2 + 6e^{-2.5(t-t_a)}$ for $t_a < t < t_b$ we already know the bounds. At $t=t_a$ the $V_c = 8V$ & @ $t=t_b$ the $V_c = 6V$. we can check the first assumption easy by plugging in $t=t_a$ to the equation

$$2 + 6e^{-2.5(t_a-t_a)} = 8$$

$$V_c(t_a) = 2 + 6e^0 = 8$$

this checks out.

So if we plug in $t=t_b$ we get the form of what is needed to be found.

$$\therefore b = 2 + 6e^{-2.5(t_b-t_a)}$$


$$\therefore 4 = 6e^{-2.5(t_b-t_a)}$$

$$\therefore \frac{2}{3} = e^{-2.5(t_b-t_a)}$$

$$\therefore \ln\left(\frac{2}{3}\right) = \ln\left(e^{-2.5(t_b-t_a)}\right) = -2.5(t_b-t_a)/\cancel{2.5}$$

$$\therefore (t_b - t_a) \approx 0.162 \text{ s or } 162 \text{ ms}$$

Given the ckt:

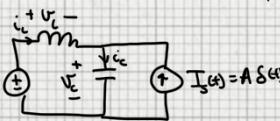

$$i_L(0) = 0^+ \quad \underline{V_C(0^-) = 0^+}$$

Find $i_L(0)$ & $V_C(0)$

$$\begin{array}{lll} \text{KCL} & \text{KVL} & \text{Component eqn} \\ i_L + I_s = i_C & V_s = V_L + V_C & i_C = C V_C' \\ i_L = i_C - A \delta(t) & & i_C' = C V_C'' \\ i_L' = i_C' - A \delta'(t) & & V_L = L i_L' \end{array}$$

$$\begin{aligned} V_s(t) &= L i_L' + V_C = L [C V_C'' - A \delta'(t)] + V_C \\ \therefore V_C'' + \frac{V_C}{LC} &= \frac{V_s(t)}{LC} + \frac{A}{LC} \delta'(t) \end{aligned}$$

Because I don't know how to handle $\delta'(t)$ in time domain, I am going to use the Laplace Transform

Recall

$$\mathcal{L}\{f(t)\} = F(s)$$

$$\mathcal{L}\{f'(t)\} = sF(s) - f(0)$$

$$\mathcal{L}\{f''(t)\} = s^2 F(s) - sf(0) - f'(0)$$

$$\therefore \mathcal{L}\left\{ V_C'' + \frac{V_C}{LC} \right\} = s^2 V_C(s) - sV_C(0) - V_C'(0) + \frac{V_C(s)}{LC}$$

where $V_C(0) = 0$

$$\text{and } i_C = i_L + A \delta(t) = C V_C'$$

$$\therefore V_C'(0) = \frac{i_C(0)}{C} + \frac{A}{C} \delta(0)$$

$$\therefore V_C'(0) = \frac{A}{C}$$

$$\therefore s^2 V_C(s) - s^2 \frac{0}{C} - \frac{A}{C} + \frac{V_C(s)}{LC} = V_C(s) \left[s^2 + \frac{1}{LC} \right] - \frac{A}{C}$$

$$\therefore \mathcal{L}\left\{ \frac{V}{LC} \delta(t) + \frac{A}{C} \delta'(t) \right\} = \frac{V}{LC} + s \frac{A}{C}$$

$$\text{so, } V_C(s) \left[s^2 + \frac{1}{LC} \right] - \frac{A}{C} = \frac{A}{C} s + \frac{V}{LC}$$

$$\therefore V_C(s) = \frac{\frac{A}{C} s + \frac{V}{LC}}{s^2 + \frac{1}{LC}} = \frac{A}{C} \frac{s}{s^2 + \frac{1}{LC}} + \frac{\frac{V}{LC}}{s^2 + \frac{1}{LC}}$$

Using a Laplace Transform Table

$$f(t) \leftrightarrow F(s)$$

$$\delta(t) \leftrightarrow 1$$

$$u(t) \leftrightarrow \frac{1}{s}$$

$$e^{-at} u(t) \leftrightarrow \frac{1}{s+a}$$

$$\sin(\omega t) u(t) \leftrightarrow \frac{\omega}{s^2 + \omega^2}$$

$$\cos(\omega t) u(t) \leftrightarrow \frac{s}{s^2 + \omega^2}$$

$$\mathcal{L}^{-1}\left\{ \frac{A}{C} \frac{s}{s^2 + \frac{1}{LC}} \right\} \rightarrow \frac{A}{C} \int_0^\infty \left\{ \frac{s}{s^2 + \frac{1}{LC}} \right\} dt = \frac{A}{C} \cos\left(\frac{t}{\sqrt{LC}}\right) u(t)$$

$$\mathcal{L}^{-1}\left\{ \frac{V+AL}{LC} \cdot \frac{\sqrt{LC}}{s^2 + \frac{1}{LC}} \right\} = \frac{V+AL}{LC} \cdot \sin\left(\frac{t}{\sqrt{LC}}\right) u(t)$$

$$\mathcal{L}^{-1}\left\{ V_C(s) \right\} = V_C(t) u(t)$$

Therefore, for $t \geq 0$

$$\begin{aligned} V_C(s) &= \frac{A}{C} \cos\left(\frac{t}{\sqrt{LC}}\right) + \frac{V+AL}{LC} \sin\left(\frac{t}{\sqrt{LC}}\right) \\ \therefore V_C(s) &= \frac{A}{C} \end{aligned}$$

$$i_L(t) = C V_C'(t) - A \delta(t)$$

where

$$\begin{aligned} V_C'(t) &= -\frac{A}{LC} \sin\left(\frac{t}{\sqrt{LC}}\right) + \frac{V+AL}{LC} \cos\left(\frac{t}{\sqrt{LC}}\right) \\ V_C'(0) &= \frac{V+AL}{LC} \\ \therefore V_C'(0) &= (V_C(0))' - A \delta(0) \end{aligned}$$

$$\therefore i_L(0) = C \left(\frac{V+AL}{LC} \right) - A$$

$$i_L(0) = \frac{V}{L}$$

The frequency of this ckt comes from inside the trig.

$$\cos(\omega t) = \cos\left(\frac{t}{\sqrt{LC}}\right)$$


$$\omega = \frac{1}{\sqrt{LC}} \quad \text{where } \omega = 2\pi f$$

$$\therefore 2\pi f = \frac{1}{\sqrt{LC}}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

Delta functions are a funny function. They set i.c. conditions.

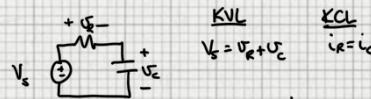Let's look @ a simple RC network. for $t \geq 0$



$$V_C(0^-) = 0^+$$

$$V_R = R \cdot i_R = R \cdot \dot{V}_C = R C \dot{V}_C'$$

$$i_C = C \cdot V_C'$$

$$\therefore V_s = R C V_C' + V_C \quad \text{where } V_s = V_s(t)$$

$$\therefore V_C' + \frac{V_C}{RC} = \frac{V_s}{RC} = \frac{V_s(t)}{RC}$$

$$\mathcal{L}\left\{ V_C' + \frac{V_C}{RC} \right\} = sV_C(s) - V_C(0) + \frac{V_s(s)}{RC}$$

$$\mathcal{L}\left\{ \frac{V}{RC} \delta(t) \right\} = \frac{V}{RC}$$

$$\therefore V_C(s) = \frac{V}{RC} \left(\frac{1}{s+RC} \right) \quad \text{Recall: } \frac{f(t)}{s+a} \leftrightarrow \frac{1}{s+a}$$

$$\therefore V_C(t) = \frac{V}{RC} e^{-\frac{t}{RC}} u(t)$$

and for $t \geq 0$

$$V_C(t) = \frac{V}{RC} e^{-\frac{t}{RC}}$$

Another way to look @ an impulse (delta) function as the driving function is to analyze a step response and take the derivative of that.

step function

$$\text{Recall: } V_C' + \frac{V_C}{RC} = u(t) \quad \text{where } V_C(0) = 0^+$$

$$\therefore \mathcal{L}\{u\} \rightarrow sV_C(s) + \frac{V_C(s)}{RC} = \frac{1}{s} V_C(s)$$

$$\therefore V_C(s) \left[s + \frac{1}{RC} \right] = \frac{1}{s} \quad V_C(s) = \frac{1}{s + \frac{1}{RC}}$$

$$\therefore \mathcal{L}\{u\} \rightarrow V_C(t) = u(t) - e^{-\frac{t}{RC}}$$

& for $t \geq 0$


$$V_C(t) = 1 - e^{-\frac{t}{RC}} \quad \text{step response}$$

to find impulse response just take a derivative of the step response.

$$V_C(t) = \frac{1}{RC} e^{-\frac{t}{RC}}$$

what's happening?

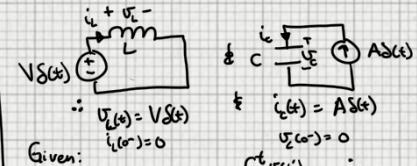well the current source is charging the capacitor and the voltage source is charging the inductor.



$$\therefore V_C(0) = V_s(0) \quad i_L(0) = 0 \quad V_C(0) = 0$$

$$\text{Given: } V_C = L i_L \quad \text{or} \quad i_L = \int_0^t \frac{V_C(t')}{L} dt + i_L(0)$$

$$\therefore i_L(t) = \int_0^t \frac{V_C(t')}{L} dt + i_L(0)$$

$$i_L(t) = \frac{V}{L}$$


if you don't understand $\delta(t)$

it is defined as having an area of 1 at $t=0$. Therefore, the current is following a voltage source that has a zero rise & zero fall time. It is this energy that is setting the direction of the current. Just like the current source is setting the voltage on the capacitor.

$$V_C(t) = \int_0^t \frac{A}{C} \delta(t') dt + V_C(0)$$

$$V_C(0) = \frac{A}{C}$$

Given the ckt:

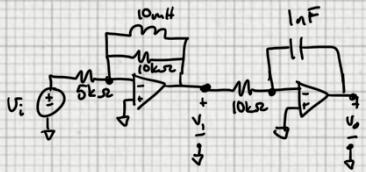


$$\text{assume } i_c(0^-) = 0^+ \quad v_c(0^-) = 0^V$$

$$\text{and } V_i = 2u(t)$$

and ideal op-amps. find V_1 & V_0 $t > 0$

Stage 1

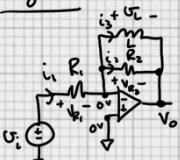

we must solve the ODE before being able to find V_0

<u>KCL</u> $i_1 + i_2 + i_3 = 0$	<u>KVL</u> $V_i = V_{R_1}$	<u>Component Eqs</u> $U_{R_{in}} = R_i \cdot i_{R_i}$
$i_1 = i_{R_1}$	$U_{R_2} = U_i = -V_0$	$U_{L_i} = L \cdot i_{L_i}'$
$i_2 = i_{R_2}$		
$i_3 = i_L$		

$$\therefore \frac{U_{R_1}}{R_1} = \frac{U_{R_2}}{R_2} + i_L, \text{ where } U_{R_2} = U_L = L \cdot i_L'$$

$$\hookrightarrow \frac{U_{R_1}}{R_1} = \frac{L}{R_2} i_L' + i_L \rightarrow i_L' + \frac{R_2}{L} i_L = \frac{R_2}{R_1} \cdot \frac{U_i}{L}$$

$$\mathcal{L}\{i_L' + \frac{R_2}{L} i_L\} = S I_L(s) - i_L(0)^0 + \frac{R_2}{L} \mathcal{I}_i(s)$$

$$\mathcal{L}\left\{\frac{R_2}{R_1 L} \cdot 2u(t)\right\} = \frac{2R_2}{R_1 L} \cdot \frac{1}{s}$$

$$\therefore I_L(s) \left[s + \frac{R_2}{L} \right] = \frac{2R_2}{R_1 L} \cdot \frac{1}{s}$$

$$\therefore I_L(s) = \frac{2R_2}{R_1 L} \cdot \frac{1}{s(s + \frac{R_2}{L})} = \frac{2R_2}{R_1 L} \left(\frac{\frac{R_2}{L}}{s} - \frac{\frac{R_2}{L}}{s + \frac{R_2}{L}} \right)$$

used partial fraction decomp.

$$\mathcal{L}^{-1}\left\{ I_L(s) = \frac{2R_2}{R_1 L} \left[\frac{1}{s} - \frac{1}{s + \frac{R_2}{L}} \right] \right\}$$

using Laplace Tables

$$f(t) \leftrightarrow F(s)$$

$$w(t) \leftrightarrow \frac{1}{s}$$

$$e^{at} \leftrightarrow e^{-as}$$

$$e^{at} u(t) \leftrightarrow s-a$$

$$\therefore i_L(t) = \frac{2R_2}{R_1 L} \left(\frac{1}{s} \cdot u(t) - \frac{1}{s + \frac{R_2}{L}} e^{-\frac{R_2 t}{L}} \right)$$

for $t > 0$

$$i_L(t) = \frac{2}{R_1} - \frac{2}{R_1} e^{-\frac{R_2 t}{L}} \quad \& \quad i_L'(t) = \left(-\frac{2}{R_1} \right) \left(-\frac{R_2}{L} \right) e^{-\frac{R_2 t}{L}}$$

$$\therefore V_L(t) = L \cdot i_L'(t) = L \left(\frac{2R_2}{R_1 L} \right) e^{-\frac{R_2 t}{L}}$$


$$V_L(t) = \frac{2R_2}{R_1} e^{-\frac{R_2 t}{L}} \quad \& \quad V_0 = -V_L$$

$$\therefore V_0(t) = -\frac{2R_2}{R_1} e^{-\frac{R_2 t}{L}} \quad \& \quad V_0(t) = -4e^{-10t}$$

Now to Solve Stage 2

we use the same approach but apply the capacitor eqn:

$$i_C = C V_C'$$

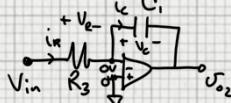

KCL

$$i_{R_3} = i_{C_1}$$

KVL

$$V_{R_3} = V_{in}$$

$$V_{C_1} = -V_{O_2}$$

Component Eqs

$$V_{R_3} = R_i \cdot i_{R_3}$$

$$i_C = C V_C'$$

\therefore

$$\frac{U_{R_3}}{R_3} = C_1 V_{C_1}' \rightarrow \frac{V_{in}}{R_3} = C_1 V_{C_1}'$$

$$V_{C_1}' = \frac{U_{in}}{R_3 C_1}$$

Homogeneous

$$U_{C_1H} = K_1 e^{\frac{-st}{C_1}} = K_1$$

Characteristic eqn
 $s=0$

Particular

need to know the input.

$$U_i = -\frac{2R_2}{R_1} e^{-\frac{R_2 t}{L}} \quad \& \quad U_{C_1P} = A e^{-\frac{R_2 t}{L}}$$

$$\therefore -\frac{2R_2}{L} e^{-\frac{R_2 t}{L}} = -\frac{2R_2}{R_1 R_3 C_1} e^{-\frac{R_2 t}{L}}$$

$$\therefore -\frac{2R_2}{L} = -\frac{2R_2}{R_1 R_3 C_1} \rightarrow A = \frac{2L}{R_1 R_3 C_1}$$

$$\therefore U_{C_1}(t) = U_{C_1H} + U_{C_1P} = K_1 + \frac{2L}{R_1 R_3 C_1} e^{-\frac{R_2 t}{L}}$$

where $U_{C_1}(0) = 0$ \therefore



$$0 = K_1 + \frac{2L}{R_1 R_3 C_1} e^0 \rightarrow K_1 = -\frac{2L}{R_1 R_3 C_1}$$

$$\therefore U_{C_1}(t) = \frac{2L}{R_1 R_3 C_1} \left(e^{-\frac{R_2 t}{L}} - 1 \right)$$

$$\boxed{U_{O_2} = -U_{C_1} = \frac{2L}{R_1 R_3 C_1} \left(1 - e^{-\frac{R_2 t}{L}} \right)}$$

$$\text{given the values} \rightarrow U_{O_2} = \frac{2 \cdot 10^{-2}}{S \cdot 10^3 / 10} (1 - e^{-10t}) = \frac{4}{10} (1 - e^{-10t})$$

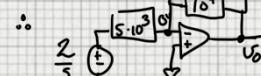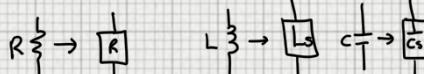If you know the Laplace Transfer for components let's analyze this: (note: w/out i.c. transforms)



$$10^2 \cdot s // 10^4 = \frac{10^2 s}{10^2 (s + 10^6)} = \frac{10^4 s}{s + 10^6}$$

Using the negative feedback general equation

$$V_o = \left(1 + \frac{Z_o}{Z_i} \right) V_2 - \left(\frac{Z_o}{Z_i} \right) V_i$$

where

$$V_2 = 0 \quad Z_o = \frac{10^4 s}{s + 10^6} \quad Z_i = 5 \cdot 10^3$$

$$V_i = \frac{2}{s}$$

$$V_o(s) = -\frac{10^4 s}{5 \cdot 10^3 \cdot (s + 10^6)} \cdot \frac{2}{s} = -\frac{4 \cdot 10^4 s}{10^4 s \cdot (s + 10^6)}$$

$$V_o(s) = \frac{-4}{(s + 10^6)} \rightarrow V_o(t) = -4e^{-10t} \quad \text{for } t \geq 0$$

for the second stage



using the same eqn we get:

$$V_2 = 0 \quad Z_o = \frac{10^9}{s}$$

$$V_i = \frac{-4}{s + 10^6} \quad Z_i = 10^4$$

$$\therefore V_o(s) = \frac{-10^9}{s 10^4} \left(\frac{-4}{s + 10^6} \right)$$

$$\hookrightarrow V_o(s) = \frac{4 \cdot 10^5}{s(s + 10^6)} = \frac{A}{s} + \frac{B}{s + 10^6}$$

$$A = 4/10 \quad B = -4/10$$


$$\therefore V_o(s) = \frac{4}{10} \cdot \frac{1}{s} - \frac{4}{10} \cdot \frac{1}{s + 10^6}$$

$$\left\{ \begin{array}{l} V_o(t) = \frac{4}{10} u(t) - \frac{4}{10} e^{-10t} \\ \text{for } t \geq 0 \end{array} \right.$$

$$V_o(t) = \frac{4}{10} - \frac{4}{10} e^{-10t} = \frac{4}{10} \left(1 - e^{-10t} \right)$$

We see how powerful the Laplace technique is and how quickly a solution can be found for basic driving functions.

Given the ckt:

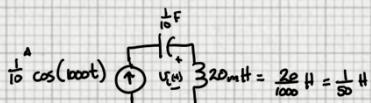

$$V_L(t) = 0^*$$

Determine $V_L(t)$.

Multiple ways can be used to solve this problem.

① Time domain

$$V_L(t) = L \cdot i_L'(t) \quad \text{where } \frac{KCL}{i_L} = i_L = \frac{1}{10} \cos(100t)$$

$$\therefore V_L(t) = \frac{1}{500} \frac{d}{dt} (\frac{1}{10} \cos(100t)) = \frac{1}{500} \cdot (-\sin(100t) \cdot 100) = -2 \sin(100t)$$

$$V_L(t) = -\frac{1000}{500} \cdot \sin(100t) = -2 \sin(100t)$$

$$\therefore V_L(t) = -2 \sin(100t)$$

② Phasor technique



KCL still shows all currents to be the same. Therefore,

$$V_L(w) = Z(w) \cdot I_L(w) = j(1000 \frac{1}{50}) \cdot \frac{1}{10}$$

$$V_L(w) = j \frac{1000}{500} = j2$$

$$|V_L(w)| = 2 \quad \angle V_L(w) = \frac{\pi}{2}$$

$$\therefore V_L(t) = |V_L(w)| \cdot \cos(1000t + \angle V_L(w))$$

$$V_L(t) = 2 \cos(1000t + \frac{\pi}{2})$$

We know from Trig that

$$\cos(wt + \frac{\pi}{2}) = -\sin(wt)$$

$$\therefore V_L(t) = -2 \sin(1000t)$$

Note: Laplace Transform and Phasor technique are the same in this case:

- sinusoidal input
- no initial conditions
- no transient information (for this case that current source has been on for all time)

Given the ckt:



Set open for a very long time and closes at t=0. Find $i_L(0^+)$


Analysis of the inductor shows $i_L(0^-) = 0^*$ due to no path for current.

$\therefore i_L(0^+) = 0^*$. The KCL shows

$$0.03^* = i_L(t) + i_R(t) = i_L(0^+) + i_R(0^+)$$

$$\therefore i_R(0^+) = 0.03^*$$


Given the ckt:

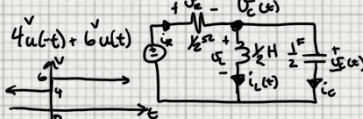

Find $i_L(t)$ for $t > 0$.

We see the source was 4^* for all time before zero. Assuming the states for inductor and capacitor; (the inductor = short, capacitor = open)

\therefore ckt for $t < 0$ becomes

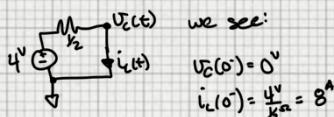

Now we know the initial conditions (i.e.) let's solve this ckt:

① Using Diff Eq.

KVL

$$V_{in} = V_R + V_L$$

$$V_L = V_L$$

KCL

$$i_R = i_L + i_C$$

$$V_R = R \cdot i_R$$

Component eqns

$$V_L = L \cdot i_L'$$

$$i_C = C \cdot V_C$$

$$\text{we see } V_R = R \cdot i_R = R(i_L + i_C)$$

$$\therefore V_{in} = R \cdot i_L + R \cdot i_C + L \cdot i_L'$$

$$\therefore V_{in} = R \cdot i_L + R \cdot C \cdot V_C + L \cdot i_L'$$

$$\therefore V_{in} = R \cdot i_L + R \cdot C \cdot L \cdot i_L'' + L \cdot i_L'$$

$$\therefore V_{in} = i_L'' + \frac{1}{RC} i_L' + \frac{1}{L} i_L$$

$$\text{RLC} \quad 48 = i_L'' + 4i_L' + 4i_L \quad \leftarrow R=L=C=\frac{1}{2}$$

Homogeneous Soln

characteristic eqn

$$s^2 + \frac{1}{R} s + \frac{1}{L} = 0 \rightarrow s^2 + 4s + 4 = 0$$

$$\therefore (s+2)(s+2) = 0 \quad S_{1,2} = 2$$

repeated roots needs special handling

$$\therefore i_{L,H} = K_1 e^{-2t} + K_2 t e^{-2t}$$

Particular Solution

Given a constant driving function

$$i_{L,P} = A \quad \therefore i_{L,P}' = i_{L,P}'' = 0$$

plugging back in and solving for A

$$48 = 0^0 + 4 \cdot 0^0 + 4 \cdot A$$

$$\therefore A = 12$$

General Soln:

$$i_L(t) = K_1 e^{-2t} + K_2 t e^{-2t} + 12^*$$

using i.c.

$$i_L(0^+) = 8^* = K_1 e^{0^*} + K_2 (0^*) e^{0^*} + 12^*$$

$$\therefore K_1 = -4^*$$

To use the second ic. we need to take equation over to $V_L(t)$. Recall:

$$V_L(t) = V_L = L \cdot i_L'$$

$$\therefore V_L(t) = \frac{1}{2} \frac{d}{dt} (K_1 e^{-2t} + K_2 t e^{-2t} + 12^*)$$

$$\therefore V_L(t) = \frac{1}{2} (2K_1 e^{-2t} + K_2 (e^{-2t} - 2te^{-2t}))$$

$$\text{given } V_L(0) = 0 = \frac{1}{2} (-2K_1 + K_2)$$

$$\therefore K_2 = 2K_1 \Rightarrow 2(-4) = -8$$

and now plugging back in coefficients we find:

$$i_L(t) = -4e^{-2t} - 8te^{-2t} + 12 \quad \therefore V_L(t) = 8te^{-2t}$$

Because of initial conditions and no frequency input

Phasor technique cannot be used. Also Phasor technique only yields steady state response & does not have transient info.

② Laplace Technique

Before jumping straight into it, let's go over some Laplace info.

You are using the unilateral Laplace transform. This means the transforms are for functions multiplied by $u(t)$. Here is a quick table:

$f(t)$	\rightleftharpoons	$F(s)$
$s(t)$	\rightleftharpoons	1
$\frac{1}{t}$	\rightleftharpoons	$\frac{1}{s}$
e^{-at}	\rightleftharpoons	$\frac{1}{s+a}$
$\sin(wt)$	\rightleftharpoons	$\frac{w}{s^2 + w^2}$
$\cos(wt)$	\rightleftharpoons	$\frac{s}{s^2 + w^2}$
$t^n e^{-at}$	\rightleftharpoons	$\frac{n!}{(s+a)^{n+1}}$

We like Laplace because it can handle initial conditions and aperiodic driving functions as well.

$$f(t) \rightleftharpoons F(s)$$

$$g(t) \rightleftharpoons \frac{1}{s} F(s)$$

$$h(t) \rightleftharpoons \frac{1}{s} F(s)$$

$$i(t) \rightleftharpoons \frac{1}{s} F(s)$$

$$j(t) \rightleftharpoons \frac{1}{s} F(s)$$

$$k(t) \rightleftharpoons \frac{1}{s} F(s)$$

$$l(t) \rightleftharpoons \frac{1}{s} F(s)$$

Given the time domain eqn:

$$i_L'' + 4i_L' + 4i_L = 48 \quad \text{when } i_L(0) = 8$$

$$i_L'(0) = L \cdot V_L(0)$$

$$i_L'(0) = L \cdot V_C(0) = 0$$

taking the Laplace of this eqn we get

$$\left[s^2 I_L(s) - s i_L(0) - i_L'(0) \right] + 4 \left[s I_L(s) - i_L'(0) \right] + 4 I_L(s) = \frac{48}{s}$$

$$= \frac{48}{s}$$

$$I_L(s) [s^2 + 4s + 4] - 8s - 32 = \frac{48}{s}$$

$$\therefore I_L(s) = \frac{\frac{48}{s} + 8s + 32}{(s+2)^2} = \frac{48 + 8s^2 + 32s}{s(s+2)^2}$$

$$\therefore I_L(s) = \frac{8(s^2 + 4s + 6)}{s(s+2)^2} = \frac{A}{s} + \frac{B}{(s+2)^2} + \frac{C}{s+2}$$

$$\text{where } A = \frac{8(s^2 + 4s + 6)}{(s+2)^2} \Big|_{s=0} = \frac{48}{4} = 12$$

$$B = \frac{8(s^2 + 4s + 6)}{s} \Big|_{s=-2} = \frac{8(-2)}{-2} = -8$$

$$C = \left[\frac{8(s^2 + 4s + 6)}{s(s+2)} - \frac{12}{s+2} - \frac{8s}{(s+2)^2} \right] \Big|_{s=1}$$

choose any value
not 0 or -2

$$\therefore C = \left[\frac{8(11)}{3} - 12(3) + \frac{8}{3} \right] = \frac{96}{3} - 36$$

$$C = -4$$

$$\therefore I_L(s) = \frac{12}{s} - \frac{8}{(s+2)^2} - \frac{4}{s+2}$$

$\mathcal{L}^{-1}\{ \}$


$$\therefore i_L(t) = 12u(t) - 4e^{-2t}u(t) - 8te^{-2t}u(t)$$

for $t \geq 0$

$$\boxed{i_L(t) = 12 - 4e^{-2t} - 8te^{-2t}} \quad \checkmark$$

To save time:

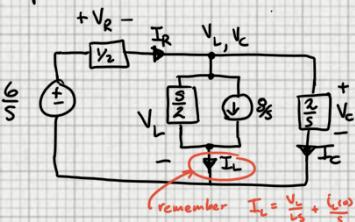Let's build the ckt from scratch straight into the Laplace domain.



Therefore,

$$V_R = \frac{6}{s} = V_R + V_L \quad \& \quad I_R = \frac{\frac{6}{s} - V_L}{R}$$

$$\therefore I_R = \frac{12}{s} - 2V_L$$

$$I_C = C_s V_C = C_s V_L = \frac{s}{2} V_L$$

$$I_L = \frac{V_L}{Ls} + \frac{8}{s} = \frac{2}{s} V_L + \frac{8}{s}$$

∴ plugging all this into KCL:

$$\frac{12}{s} - 2V_L = \underbrace{\frac{2}{s} V_L + \frac{8}{s}}_{I_L} + \underbrace{\frac{s}{2} V_L}_{I_C}$$

$$V_L \left(2 + \frac{2}{s} + \frac{s}{2} \right) = \frac{12}{s} - \frac{8}{s} = \frac{4}{s}$$

$$V_L \left(\frac{s^2 + 4s + 4}{2s} \right) = \frac{4}{s}$$

$$V_L = \frac{8}{(s+2)^2} = V_C$$

$$\mathcal{L}^{-1} \left\{ \frac{8}{(s+2)^2} \right\} = 8te^{-2t}u(t) \quad \checkmark$$

Recall

$$I_L = \frac{V_L}{Ls} + \frac{i_L(s)}{s} = \frac{8}{(s+2)^2} \cdot \frac{2}{s} + \frac{8}{s}$$

$$I_L = \frac{16}{s(s+2)^2} + \frac{8}{s} = \frac{16 + 8(s^2 + 4s + 4)}{s(s+2)^2}$$

$$I_L = \frac{8s^2 + 32s + 48}{s(s+2)^2} = \frac{8(s^2 + 4s + 6)}{s(s+2)^2}$$

$$\therefore I_L = \frac{A}{(s+2)} + \frac{B}{(s+2)^2} + \frac{C}{s}$$

$$B = \frac{8(s^2 + 4s + 6)}{s} \Big|_{s=-2} = \frac{8(4-8+6)}{-2} = -8$$

$$C = \frac{8(s^2 + 4s + 6)}{(s+2)^2} \Big|_{s=0} = \frac{8(6)}{4} = 12$$

$$A = (s+2) \left[\frac{8(s^2 + 4s + 6)}{s(s+2)^2} - \frac{-8}{(s+2)^2} - \frac{12}{s} \right] \Big|_{s=1}$$

$$A = 3 \left[\frac{8(1+4+6)}{9} + \frac{8}{9} - 12 \right]$$

$$A = \frac{88}{3} + \frac{8}{3} - 36 = \frac{96}{3} - 36 = -4$$

$$\therefore I_L = \frac{-4}{(s+2)} - \frac{8}{(s+2)^2} + \frac{12}{s}$$

$\mathcal{L}^{-1}\{ \}$


$$i_L(t) = -4e^{-2t}u(t) - 8te^{-2t}u(t) + 12u(t)$$

for $t \geq 0$

$$\boxed{i_L(t) = -4e^{-2t} - 8te^{-2t} + 12} \quad \checkmark$$

KCL	KVL	Component eqns
$I_R = I_L + I_C$	$\frac{6}{s} = V_R + V_L$	$V_R = R \cdot I_R$
	$V_L = V_C$	$I_L = \frac{V_L}{Ls} + \frac{i_L(s)}{s}$
		$V_C = \frac{I_C}{Cs} + \frac{V_L}{s}$

Given the ckt:

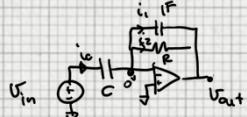

$$\text{where } V_{in} = u(t)$$

$$V_{out} = -\frac{1}{2} e^{-\frac{t}{RC}} u(t)$$

final RC to give the step response

From the op-amp rules

where

$$i_s = i_p = 0^+ \quad V_+ = V_-$$

we see

$$V_c = V_{in} - 0 = u(t)$$

$$i_c = C V_c' = C \frac{d}{dt}(u(t)) = C \delta(t)$$

The KCL shows

$$i_c = i_1 + i_2$$

$$\text{where } i_1 = (IF) \frac{d}{dt}(0 - V_{out})$$

$$i_2 = \frac{0 - V_{out}}{R}$$

$$\therefore C \delta(t) = -\frac{1}{R} (V_{out}) - \frac{V_{out}}{R}$$

$$\Rightarrow V_{out}' + \frac{V_{out}}{R} = -C \delta(t)$$

knowing that:

$$V_{c_2} = -V_{out} \quad \& \quad V_{c_2}(0) = 0^+$$

$$\text{then } V_{out+}(0) = 0^+$$

$$\underbrace{\{ \}_{s=0}}_{sV_{out}(s)} - V_{out}(0) + \frac{V_{out}(s)}{R} = -C$$

$$V_{out}(s) \left[s + \frac{1}{R} \right] = -C$$

$$V_{out}(s) = \frac{-C}{s + \frac{1}{R}}$$

$$\underbrace{\{ \}_{s=0}}_{V_{out}(t)} - V_{out}(0) e^{-\frac{t}{RC}} u(t)$$

given

$$V_{out} = -\frac{1}{2} e^{-\frac{t}{RC}} u(t)$$

$$\text{then } C = k_2$$

$$R = k_1$$

Recall:

$$V_{out}' + \frac{V_{out}}{R} = -C \delta(t)$$

$$\therefore V_{out}(0) = -C$$

& the O.D.E. becomes

$$V_{out}' + \frac{V_{out}}{R} = 0$$

$$V_{out,H} = K_1 e^{st}$$

characteristic eqn:

$$s + \frac{1}{R} = 0$$

$$s = -\frac{1}{R}$$

$$\therefore V_{out,H} = K_1 e^{-\frac{t}{R}}$$

given that now no particular,

$$V_{out} = K_1 e^{-\frac{t}{R}}$$

using new i.c.

$$V_{out}(0) = -C = K_1 e^{-\frac{t}{R}}$$

$$\therefore K_1 = -C$$

$$\& V_{out} = -Ce^{-\frac{t}{R}}$$


just like the Laplace transform

$$\therefore C = \frac{1}{2} \quad R = \frac{1}{4}$$

without solving using Laplace
a trick must be invoked.

since no initial conditions
the $\delta(t)$ will set one
and there will be no particular
solution only a homogeneous
solution.

Given a Black Box

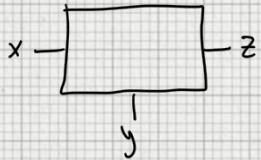

We know an RLC ckt is inside; one of each component.

Given $C = 1\mu F$



Ohm reading are as follows:

$$R_{xy} = \infty$$

$$R_{xz} = 40\Omega$$

$$R_{yz} = \infty$$

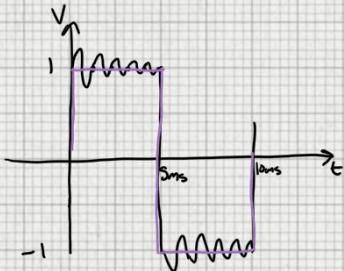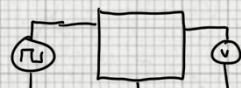Applying a square wave @ X-Y yields a voltage reading of Z-Y



so what do we know

For sure

$$x \text{---} M \text{---} z$$

$$\frac{1}{Y}$$

Therefore
these can be
switched

$$x \text{---} M \text{---} M \text{---} z$$

$$\frac{1}{Y}$$

we also know
the ckt resonates
so all 3
components
must be connected

we also see the
O/P of V_{zy} follows
the I/P therefore
 V_{z-y} must be
the capacitor
voltage.

we find the R to be equal
to 40Ω because of the
Ohmmeter reading.

we also see the O/P voltage
resonates. Therefore this must
be an under damped system.

We know the RLC series ckt is of the form:

$$V_C'' + \frac{R}{L}V_C' + \frac{1}{LC}V_C = V_{in}$$

 and if under damped
 then $\frac{1}{LC} > \left(\frac{R}{2L}\right)^2$

and

$$V_C(t) = e^{-\sigma t} (K_1 \cos(\omega_0 t) + K_2 \sin(\omega_0 t))$$

where

$$\omega_0^2 = \frac{1}{LC} \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$2\sigma = \frac{R}{L} \rightarrow \sigma = \frac{R}{2L}$$

$$\therefore V_C(t) = e^{-\frac{Rt}{2L}} (K_1 \cos(\frac{\omega_0 t}{\sqrt{LC}}) + K_2 \sin(\frac{\omega_0 t}{\sqrt{LC}}))$$

2 ways to solve for L.

1) if we assume $5\text{ms} \approx 4T$

then

$$4\left(\frac{2L}{R}\right) \approx 5 \times 10^{-3}$$

$$\frac{8L}{40} \approx 5 \times 10^{-3} \rightarrow L \approx 25\text{ mH}$$

or

2) Assume there are 5 periods in
5 ms therefore $T = 1\text{ms}$

from the sinusoids we get

$$\omega = \frac{1}{\sqrt{LC}} = 2\pi f = \frac{2\pi}{T}$$

$$\therefore \frac{1}{\sqrt{L \cdot 10^{-6}}} \approx \frac{2\pi}{10^{-3}}$$

$$\frac{1}{L \cdot 10^{-6}} \approx \frac{4\pi^2}{10^{-6}} \approx 39.87$$

$$L \approx \frac{10^{-6}}{39.87} \cdot \frac{1}{4\pi^2} \approx 25\text{ mH}$$


What does V_{xz} look like
w/ the same I/P?

Well


$$V_{xy} = V_{xz} + V_{zy}$$

$$\therefore V_{xz} = V_{xy} - V_{zy}$$

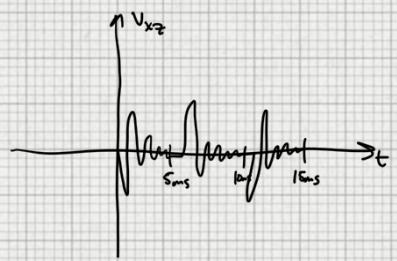so you just need to
subtract the 2 signals &
you will get something like



Given

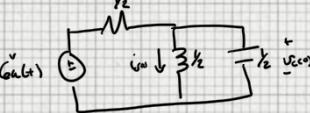

Given
 $i_L(t) = 9^A$ solve for
 $V_c(t) = 1^V$ $i_L(t) \neq V_c(t)$

The O.D.E. is:

$$i'' + \frac{1}{R} i' + \frac{1}{C} i = \frac{V_{in}}{R} - \frac{1}{C} V_c$$

or for these values

$$i'' + 4i'_L + 4i_L = 48$$

Therefore,

$$i_{LP} = K_1 e^{-2t} + K_2 t e^{-2t}$$

$$i_{LP} = 12$$

$$i_L(t) = K_1 e^{-2t} + K_2 t e^{-2t} + 12$$

$$V_c(t) = \left(\frac{K_2}{2} - K_1\right) e^{-2t} - K_2 t e^{-2t}$$

using inc.

$$i_L(0) = 9 = K_1 + 12 \quad \therefore K_1 = -3$$

$$V_c(0) = 1 = \frac{K_2}{2} - K_1 \quad \therefore K_2 = -4$$

Thus,

$$i_L(t) = -3e^{-2t} - 4te^{-2t} + 12$$

$$V_c(t) = e^{-2t} + 4te^{-2t}$$


Laplace Transform is:

$$I_L(s) = -\frac{3}{s+2} - \frac{4}{(s+2)^2} + \frac{12}{s} = \frac{9s^2 + 38s + 48}{s(s+2)^2}$$

$$\text{or } -\frac{3s+10}{(s+2)^2} + \frac{12}{s}$$

$$V_c(s) = \frac{1}{s+2} + \frac{4}{(s+2)^2} = \frac{5t+6}{(s+2)^2}$$

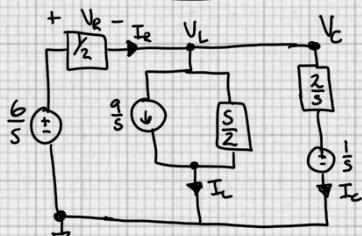When doing the transform if it doesn't yield these equations it will not yield the correct equations.



$$\begin{aligned} \text{KCL: } I_R &= I_L + I_C \\ \text{KVL: } \frac{V_R}{s} &= V_R + V_L \\ V_L &= V_C \\ \text{component eqn: } V_R &= R \cdot I_R \\ I_L &= \frac{V_R}{Ls} + \frac{i_L(t)}{s} \\ V_C &= \frac{I_C}{Cs} + \frac{V_C(t)}{s} \end{aligned}$$

$$\begin{aligned} \frac{V_R}{R} &= \underbrace{\left(\frac{V_L}{Ls} + \frac{i_L(t)}{s}\right)}_{I_L} + \underbrace{\left(CsV_C + Cv_C(t)\right)}_{I_C} \\ \frac{6}{s} - V_C &= \frac{V_L}{Ls} + \frac{i_L(t)}{s} + CsV_C + Cv_C(t) \end{aligned}$$

$$\frac{12}{s} - 2V_C = \frac{2V_L}{s} + \frac{9}{s} + \frac{sV_C}{2} - \frac{1}{2}$$

Therefore,

$$\frac{2g}{25} - \frac{12}{25} + \frac{S}{2s}$$

$$V_C \left(\frac{S}{2} + \frac{2}{3} + 2 \right) = \frac{12}{s} - \frac{9}{s} + \frac{1}{2}$$

$$V_C \left(\frac{S^2 + 4S + 4}{2s} \right) = \frac{S+6}{2s}$$

$$V_C = \frac{S+6}{(s+2)^2} \quad \checkmark$$

we know from earlier that

$$\int \{ e^{-2t} + 4t e^{-2t} \} = \frac{8t+6}{(s+2)^2}$$

For I_L we know

$$V_L = V_C = \frac{S+6}{(s+2)^2}$$

$$\therefore I_L = \frac{V_L}{Ls} + \frac{i_L(t)}{s}$$

$$\therefore I_L = \frac{2}{s} \left(\frac{S+6}{(s+2)^2} \right) + \frac{9}{s}$$

$$\Rightarrow = \frac{2s+12 + 9s^2 + 36s + 36}{s(s+2)^2}$$

$$I_L = \frac{9s^2 + 38s + 48}{s(s+2)^2} \quad \checkmark$$

we see from earlier that

$$\int \{ -3e^{-2t} - 4te^{-2t} + 12 \} = \frac{9s^2 + 38s + 48}{s(s+2)^2}$$

This example is a demonstration of applying the transform technique and using regular resistance techniques on impedance blocks and finding the equivalence of the solution in lieu of solving O.D.E.



Things to watch out for:

- simple algebra mistakes.
- incorrect transform assumptions

remember $I_L = \frac{V_L}{Ls} + \frac{i_L(t)}{s}$

$$V_C = \frac{I_C}{Cs} + \frac{V_C(t)}{s}$$

this looks like

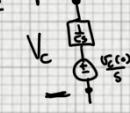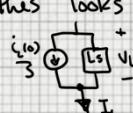

- Also be careful when taking partial fraction decomposition values.

- After each transform & inverse transform see if your circuit behaves correctly.

- Does it satisfy initial conditions (i.c.)?

- Does the system respond as it should? (underdamped, overdamped, etc.)

- Does it come to the correct steady state? (does it settle or does it oscillate?)

Remember,

Laplace yields

- transient & steady state info
- can handle initial conditions (i.c.)
- can handle sinusoids, DC, exponential & pulse signals for inputs

- You are using a unilateral Laplace Transform, which means all functions of time are $t \geq 0$. When inverse Laplace transforms are taken (even if the table isn't showing it) every function has a $u(t)$ attached to it.

Phasor Technique (Fourier Transform) is the way simplified version of the Laplace.

- $s \rightarrow j\omega$
- no initial conditions can be present
- only sinusoids for the I/P of one frequency
- only yields steady state info. (\approx transient info)