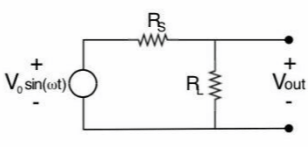


1. [40 points total] For the circuit shown below the voltage source is sinusoidal with an amplitude  $V_0$  and frequency  $\omega$ .  $R_S$  is **time varying** such that:

$R_S = R_0 + R_1 \sin(\omega_1 t)$  where  $R_0 > R_1$  (so that  $R_S$  is always positive)



- a. [15 points] Write down a relationship for  $V_{out}$  in terms of  $V_{in}$ ,  $R_L$ ,  $R_0$ , and  $R_1$ .
- b. [15 points] Further assume that  $R_0 - R_1 \gg R_L$ , and  $R_0 \gg R_L$ . Using these relationships, simplify the result from part a. and obtain a solution to first order in  $R_1$ . [Hint: this means you can't ignore  $R_1$  altogether; you may find the Taylor series for  $1/(1+x)$  for small  $x$  useful:  $1/(1+x) = (1-x)$ ].
- c. [10 points] The result from part b. should have a term of the form  $\sin(\omega t) \sin(\omega_1 t)$ . Expand this to obtain the different frequency components of  $V_{out}$  [hint: see appendix F attached]

time varying series resistor

$R_S = R_0 + R_1 \sin(\omega_1 t)$

where  $R_0 > R_1$  due to resistance cannot be negative.

Using Ohm's Law, KVL, & KCL

we get:

KVL

$V_{in} = V_{R_S} + V_{R_L}$

$V_{out} = V_{R_L}$

KCL

$I_{in} = I_{R_S} = I_{R_L}$

Ohm's Law

where  $V_{R_x} = R_x \cdot I_{R_x}$

$\therefore V_{in} = R_S \cdot \frac{I_{in}}{R_S} + V_{out}$  also  $I_{in} = \frac{V_{in}}{R_S + R_L}$

$\therefore V_{in} = R_S \left( \frac{V_{in}}{R_S + R_L} \right) + V_{out}$

$\therefore V_{out} = \left( 1 - \frac{R_S}{R_S + R_L} \right) V_{in} = \frac{R_L}{R_S + R_L} \cdot V_{in}$

Just do Voltage Divider eqn if current is the same going through all the components.

a)  $V_{out} = \frac{R_L}{R_S + R_L} \cdot V_{in}$  or  $\frac{R_L \cdot V_{in}}{R_0 + R_1 \sin(\omega_1 t) + R_L}$

using the assumptions given

$R_0 \gg R_L$  &  $R_{S,min} \gg R_L$

we can generalize our eqn:

$V_{out} \approx \frac{R_L \cdot V_{in}}{R_S} \rightarrow V_o \approx \frac{R_L V_{in}}{R_0 + R_1 \sin(\omega_1 t)}$

$\therefore V_{out} \approx R_L V_{in} \cdot \left( \frac{1}{R_0 + R_1 \sin(\omega_1 t)} \right)$

pulling out the  $R_0$  on the denominator we get

$V_{out} \approx \frac{R_L}{R_0} \cdot V_{in} \left( \frac{1}{1 + \frac{R_1}{R_0} \sin(\omega_1 t)} \right)$

using Taylor series expansion you would find for the function

$\frac{1}{1+x}$  would be approximately

equal to  $1-x$  for values of  $x$  being very small  $x \ll 1$

since  $R_0 \gg R_1$  this condition is satisfied

$\therefore \frac{1}{1 + \frac{R_1}{R_0} \sin(\omega_1 t)} \approx 1 - \frac{R_1}{R_0} \sin(\omega_1 t)$

b)  $V_{out} \approx \frac{R_L}{R_0} \cdot V_{in} \cdot \left( 1 - \frac{R_1}{R_0} \sin(\omega_1 t) \right)$

$V_{out} \approx \left( \frac{R_L}{R_0} - \frac{R_L R_1}{R_0^2} \sin(\omega_1 t) \right) V_{in}$

plugging in  $V_{in} = V_0 \sin(\omega t)$

$V_{out} \approx \left( \frac{R_L}{R_0} \sin(\omega t) - \frac{R_L R_1}{R_0^2} \sin(\omega t) \sin(\omega_1 t) \right) V_0$

Need to see Appendix F, but I'm assuming it has

$\sin(a) \cdot \sin(b) = \frac{1}{2} [\cos(a-b) - \cos(a+b)]$

$V_{out} \approx \left[ \frac{R_L}{R_0} \cdot \sin(\omega t) - \frac{R_L R_1}{2 R_0^2} [\cos(\omega_1 t - \omega t) - \cos(\omega_1 t + \omega t)] \right] V_0$

$V_{out} \approx \left[ \frac{R_L}{R_0} \sin(\omega t) - \frac{R_L R_1}{2 R_0^2} [\cos(\omega_1 - \omega)t - \cos(\omega_1 + \omega)t] \right] V_0$

$\therefore$  we look @ the terms multiplied by  $t$  in sinusoids to find freq. components

$\cos(\omega t)$  or  $\sin(\omega t)$  where  $\omega = 2\pi f$   
↑ radial frequency  
↑ frequency

$\therefore$  freq components are

c)  $\text{Freq}[V_o] = \omega + (\omega_1 - \omega) + (\omega_1 + \omega)$