
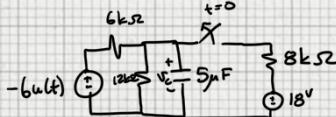


Given the ckt:

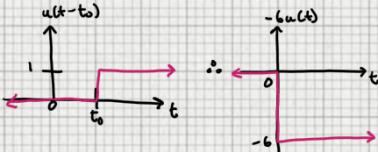


The unit step function (Heaviside) function is a piecewise function given by:

$$u(t-t_0) = \begin{cases} 1, & \text{arg}(t) \geq 0, t-t_0 \geq 0 \Rightarrow t \geq t_0 \\ 0, & \text{otherwise} \end{cases}$$



Assuming the switch is closed for a long time what is $V_C(t)$ when $t=0^+$.

Well the ckt @ $t=0^-$ is:

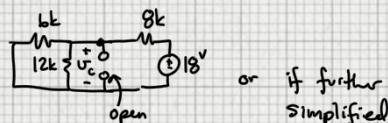

or if further simplified

$$18V \xrightarrow{\text{parallel}} \frac{6 \cdot 12}{(6+12)} k = \frac{32}{18} k = 4k$$


Since $8k \neq 4k$ share the same current we can use the voltage divider equation.

$$V_{R_2} = \left(\frac{4k}{4k+8k} \right) 18V = 6V$$

we see that given the configuration V_{R_2} is in parallel with V_C . Therefore $V_C(t=0^-) = 6V$. Since we assume voltage cannot change instantaneously across a capacitor then

$$V_C(t=0^+) = V_C(t=0^-) = 6V$$

Given the ckt:

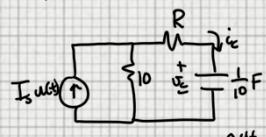


$$\left. \begin{aligned} V_C(t) &= 20 - 10e^{-0.4t} \\ i_C(t) &= 0.4e^{-0.4t} \end{aligned} \right\} \text{for } t \geq 0$$

Find the value of R.


This problem is doing nothing more than finding equivalent resistance felt by the capacitor.

Recall that any simple RC ckt has a $\tau = RC$.

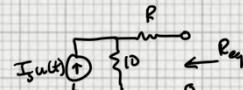We know the capacitance, we just need to find the equivalent resistance seen by capacitor. In other words:



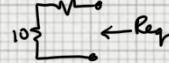When you have access to the sources, zero them out. Recall a current source with 0^A is like an open. So the ckt reduces to:



$$\therefore R_{eq} = R + 10 \Rightarrow \tau = (R + 10) \cdot 10$$

We can see from the general equation describing the voltage of a capacitor for a simple RC network:

$$V_C(t) = (V_0 - V_\infty)e^{-\frac{(t-t_0)}{\tau}} + V_\infty$$


we see that $\frac{1}{\tau} = 0.4 = \frac{1}{10}$

$$\therefore \tau = \frac{10}{4} \text{ so we equate them.}$$

$$(R + 10) \cdot \frac{1}{10} = \frac{10}{4} \rightarrow 4R + 40 = 100$$


$$\therefore 4R = 60 \rightarrow R = 15\Omega$$

Given the ckt:

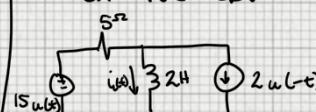


find the equation of $i_L(t)$ for $t \geq 0$.

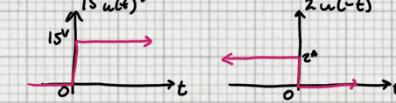The equations for the voltage & current sources look as such



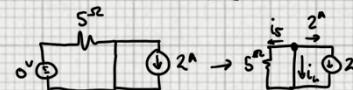we can now assume any initial states. Assuming the ckt is steady state @ negative infinity the ckt looks like



recall ohms law for resistors.


$$i_R = \frac{\Delta V_R}{R}, \text{ and since a wire drops/gains } 0^V \Delta V_R = 0^V. \text{ Due to Ohm's law } 0^V \text{ can flow}$$

through the 5Ω . So using KCL $i_5 + i_2 + 2^A = 0^A$, we see $i_2 = -2^A$.

$$\text{Our } i_0 = -2^A \quad i_C(t=0^-) = -2^A = i_C(t=0^+)$$

Since we assume current in an inductor cannot change instantaneously.

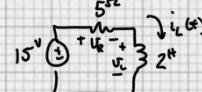Given the initial condition we can now look @ the ckt for $t \geq 0$. Which looks like:



KVL

$$15V = V_R + V_L \quad I_R = I_L$$

KCL

$$\Delta V_R = R \cdot I_R \quad \Delta V_L = L \frac{dI_L}{dt}$$

given the KCL:

$$\Delta V_R = R \cdot I_L$$

$$15 = R \cdot I_L + L I_L'$$

$$\text{or} \quad I_L' + \frac{L}{R} I_L = \frac{15}{R} \rightarrow I_L' + 2.5 I_L = 7.5$$

Homogeneous Solution

$$I_{L,H}^{(0)} = C_1 e^{-2.5t} \quad \text{where the characteristic eqn: } s + 2.5 = 0 \rightarrow s = -2.5$$

Particular Solution

$$I_{L,P} = A \quad \& \quad I_{L,P}' = 0$$

$$\therefore 0 + 2.5A = 7.5$$

$$\therefore A = \frac{7.5}{2.5} = 3$$

The general solution becomes:

$$I_L(t) = I_{L,H}^{(0)} + I_{L,P}(t) = C_1 e^{-2.5t} + 3$$

Given the initial condition $I_L(t=0^+)$ we can solve for C_1 .

$$I_L(0) = -2 = C_1 e^{0} + 3 \therefore C_1 = -5$$

and the solution becomes:

$$I_L(t) = -5e^{-2.5t} + 3$$

if we use the general current equation for an inductor in a simple LR ckt we know

$$\tau = \frac{L}{R} = \frac{2}{5} = \frac{1}{2.5} = 0.4$$

we know $t_0 = 0$

$$\text{we know } I_L(0) = -2^A \quad I_L(\infty) = \frac{V}{R} = \frac{15}{5} = 3^A$$


Plugging these values into the general equation:

$$I_L(t) = (I_{L,0} - I_{L,\infty})e^{-\frac{(t-t_0)}{\tau}} + I_{L,\infty}$$


yields the same answer but way faster.

$$I_L(t) = (-2 - 3)e^{-\frac{t}{0.4}} + 3$$

Given the ckt:

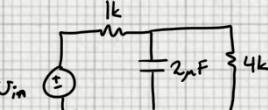
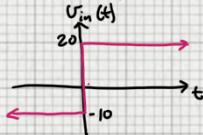
$$\text{where } V_{in}(t) = -10u(-t) + 20u(t)$$



Find the zero input response and the zero state response for $t \geq 0$.

All this is asking is,


① How does this ckt respond if the capacitor has only initial conditions and the source is zeroed out?
(zero input response) \leftarrow similar to homogeneous solution

② How does this ckt respond if the capacitor has no initial conditions and the source is the only thing exciting it?

(zero state response) \leftarrow kind of like looking \leftarrow a particular solution

Let's start w/ ①

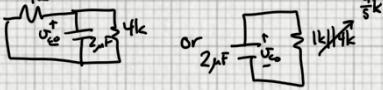if this ckt had a zeroed out source it would reduce down to



we need to find $V_c(t=0^-)$ to use as an initial condition.

@ $t = -\infty$ the capacitor acts as an open and $V_c = V_{4k}$. Using the voltage we see $V_{4k} = \left(\frac{4k}{5k}\right) \cdot (-10V)$

$$\therefore V_c(t=0^-) = -8V \Rightarrow V_{c0} = -8V$$

with a potential of $-8V$

we see the RC network will decay to $0V$ with nothing driving it. Using the general equation

$$V_c(t) = (V_{c0} - V_{c\infty}) e^{-\frac{t-t_0}{RC}} + V_{c\infty}$$

we know for this configuration

$$R = \left(\frac{4}{5}k\right) \cdot 2 \times 10^{-6} F = \frac{8}{5} \times 10^{-3}$$

$$t_0 = 0 \quad V_{c0} = -8V \quad V_{c\infty} = 0V$$

\therefore The zero input response is

The zero state response

looks at what happens when $V_{c0} = 0V$ and $V_{in}(t=0)$. The ckt for $t \geq 0$ w/ the input becomes



τ & $\frac{1}{\tau}$ is the same.
 t_0 is the same
 $V_{c0} = 0V$ & $V_{c\infty} = 20V$

using the general voltage equation for a simple RC network

$$V_c(t) = (V_{c0} - V_{c\infty}) e^{-\frac{t-t_0}{RC}} + V_{c\infty}$$


\therefore

$$V_{c, ZSR}(t) = (0 - 20) e^{-625t} + 20$$


or

$$V_{c, ZSR}(t) = 20(1 - e^{-625t})$$

Given the ckt:

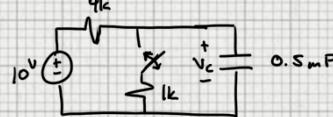

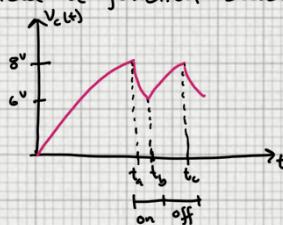Assume, $V_c(t=0) = 0V$. Also that the switch closes when $V_c = 8V$ and opens when $V_c = 6V$, to yield a function such as:



the function is given by the piecewise:

$$V_c(t) = \begin{cases} 10(1 - e^{-0.5t}), & 0 < t < t_a \text{ off} \\ 2 + 6e^{-2.5(t-t_a)}, & t_a < t < t_b \text{ on} \\ 10 - 4e^{-0.5(t-t_b)}, & t_b < t < t_c \text{ off} \\ \vdots \end{cases}$$

Find $t_b - t_a$.

You could go through multiple steps to find $t_b - t_a$ or you can literally find the time it takes for voltage to fall from $8V$ to $6V$ using the second equation in the piecewise.

Using $V_{c,out}(t) = 2 + 6e^{-2.5(t-t_a)}$ for $t_a < t < t_b$ we already know the bounds. At $t=t_a$ the $V_c = 8V$ & @ $t=t_b$ the $V_c = 6V$. we can check the first assumption easy by plugging in $t=t_a$ to the equation

$$2 + 6e^{-2.5(t_a-t_a)} = 8$$

$$2 + 6e^0 = 8$$

this checks out.

So if we plug in $t=t_b$ we get the form of what is needed to be found.

$$\therefore b = 2 + 6e^{-2.5(t_b-t_a)}$$

$$\therefore 4 = 6e^{-2.5(t_b-t_a)}$$

$$\therefore \frac{2}{3} = e^{-2.5(t_b-t_a)}$$

$$\therefore \ln\left(\frac{2}{3}\right) = \ln\left(e^{-2.5(t_b-t_a)}\right) = -2.5(t_b-t_a)/\cancel{2.5}$$

$$\therefore (t_b - t_a) \approx 0.162 \text{ s or } 162 \text{ ms}$$