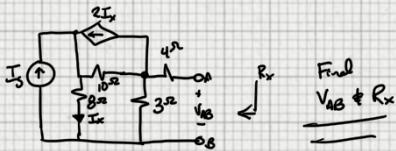


Given the ckt:



$$\therefore I_{10} = I_x - 2I_y = -I_x \quad \& \quad V_g = 8I_x$$

$$V_3 = 10(-I_x) + 8I_x = -2I_x$$

$$I = I_x + \frac{V_{g0}}{R} - \frac{2}{3}I_x \rightarrow 3I = 3I_x - 2I_x$$

$$\therefore I_x = 3I \quad \& \quad V_g = -6I$$

Therefore,

$$V = 4(I) + (-6I) = -2I$$

$$\therefore \frac{V}{I} = -2 \rightarrow R_x = \frac{V}{I} = -2\Omega$$

or you can find R_x

by finding I_{sc} , since we have already found $V_{oc} = V_{AB}$

$$R_{th} = \frac{V_{oc}}{I_{sc}}$$

The ckt becomes



KCL

$$I_s = I_x + I_3 + I_{sc}$$

$$V_g = 10 + V_3$$

$$I_s + 2I_x = I_x + I_{10}$$

$$V_g = V_4 = 4 \cdot I_{sc}$$

$$I_{10} = 2I_x + I_3 + I_{sc}$$

$$V_g = 8I_x = \frac{10(2I_x + I_3 + I_{sc})}{3} + 4I_{sc}$$

$$8I_x = 20I_x + 10 \cdot \frac{4I_{sc}}{3} + 10I_{sc} + 4I_{sc}$$

$$24I_x = 60I_x + 40I_{sc} + 30I_{sc} + 12I_{sc}$$

$$-36I_x = 82I_{sc} \rightarrow I_x = \frac{82}{36}I_{sc}$$


$$I_s = \frac{82}{36}I_{sc} + \frac{4}{3}I_{sc} + I_{sc}$$

$$36I_s = (-82 + 48 + 36)I_{sc} = 2I_{sc}$$

$$I_{sc} = 18I_s$$

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{-36I_s}{18I_s} = -2\Omega$$



Given

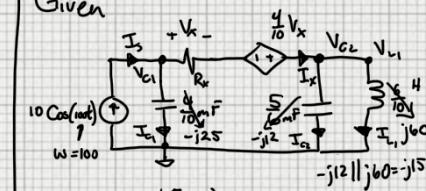


Maybe simplify to get better visual?

$$Z_1 = -j25$$

$$Z_2 = R_x \quad Z_3 = -j12 || j60 = -j15$$

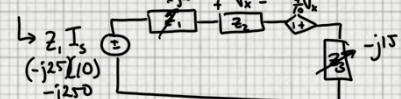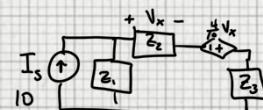

$$Z_4 = Z_1 + Z_3 = -j40$$

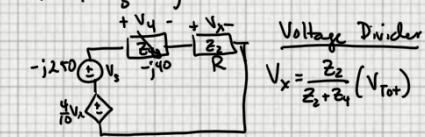

$$V_x = \frac{R}{R+j40} (V_{g0} - j250 + \frac{4}{10}V_x)$$

$$(R-j40)V_x = -jR250 + \frac{4}{10}V_x$$

$$(10-j\frac{400}{R})V_x = -j2500 + 4V_x$$

$$(6-j\frac{400}{R})V_x = -j2500$$

$$V_x = \frac{-j2500}{6-j\frac{400}{R}} \quad |V_x| = 250$$

$$\therefore \sqrt{\frac{2500}{36 + (\frac{400}{R})^2}} = 250 \rightarrow \sqrt{36 + (\frac{400}{R})^2} = 10$$

$$\therefore 36 + (\frac{400}{R})^2 = 100 \rightarrow \frac{400}{R} = \sqrt{64}$$

$$R = \frac{400}{8} = 50$$

$$\text{or } |V| = 125$$

$$\sqrt{36 + (\frac{400}{R})^2} = 20 \rightarrow 36 + (\frac{400}{R})^2 = 400$$

$$\frac{400}{R} = \sqrt{400-36} \rightarrow R = \frac{400}{\sqrt{400-36}} \approx 20.97$$

Going w/ $R = 50\Omega$

$$V_x = \frac{-j2500}{6-j\frac{400}{50}} = \frac{-j2500 \cdot j}{6-j8} = \frac{1250}{4+j3}$$

$$\therefore |V_x| = \frac{1250}{\sqrt{4^2+3^2}} = \frac{1250}{\sqrt{25}} = \frac{1250}{5} = 250$$


$$\angle V_x = \arctan(\frac{3}{4}) - \arctan(\frac{3}{4})$$

$$\therefore V_x = -\arctan(\frac{3}{4})$$

$$\therefore \text{Given } R_x = 50\Omega$$

$$V_x(t) = 250 \cos(100t - \arctan(\frac{3}{4}))$$


Given

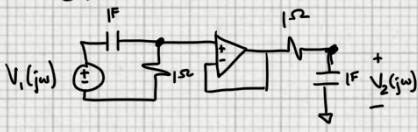

Find the transfer function

$$H(jw) = \frac{V_2(jw)}{V_1(jw)}$$

Redraw ckt using phasor technique

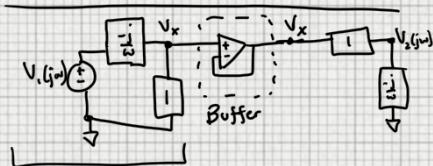

using voltage divider we see:


$$V_x = \frac{1}{1+j\omega} \cdot V_1(jw) = \frac{j\omega}{1+j\omega} V_1(jw)$$

#

$$V_2(jw) = \left(\frac{j\omega}{1+j\omega}\right) V_x = \left(\frac{1}{1+j\omega}\right) V_x$$

$$\therefore H(jw) = \frac{V_2(jw)}{V_1(jw)} = \frac{j\omega}{(1+j\omega)^2} = \frac{j\omega}{(1-\omega^2)+j2\omega}$$

Given:

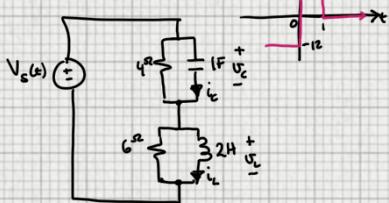

@ t=0⁻ the ckt was @ steady state

$$-12V \text{ at } i_c(0^-) = -12V \text{ at } i_L(0^-) = -3A$$


Find i_c(0⁺) & V_L(0⁺).

DON'T try and solve for equations. Use what you assume about cap & ind.

$$\text{At } t=0^+ \quad V_c(0^+) = V_c(0^-) = -12V$$

$$i_c(0^+) = i_c(0^-) = -3A$$


Looking @ ckt for t=0⁺

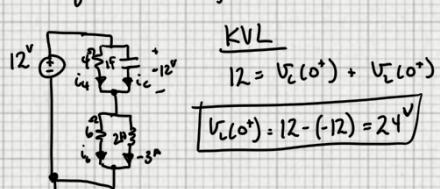

$$\text{KCL: } i_4 + i_c(0^+) = i_6 + i_L(0^+) \rightarrow \frac{V_c(0^+)}{4} + i_c(0^+) = \frac{V_L(0^+)}{6} - 3$$

$$\therefore i_c(0^+) = \frac{24}{6} - 3 - \frac{(-12)}{4} = 4 \rightarrow i_c(0^+) = 4A$$

Given:

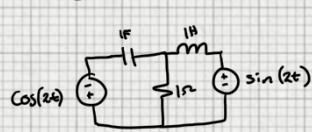

what is the average power consumed by the resistor?


Another way of asking is what is

$$\frac{1}{T} \int_0^T i_R(t) \cdot v_R(t) dt$$


$$\text{where } T = \frac{2\pi}{\omega} \text{ & } \omega = 2 \Rightarrow T = \pi$$

Since there are no initial conditions let's use Phasor technique

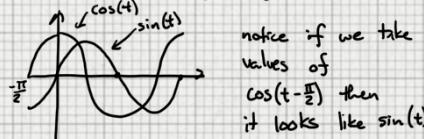∴ if cos(2t) is the starting point then sin(2t) needs to be in terms of cos(2t+π/2), looking @ the functions will give you the insight:



now putting the ckt in Phasor

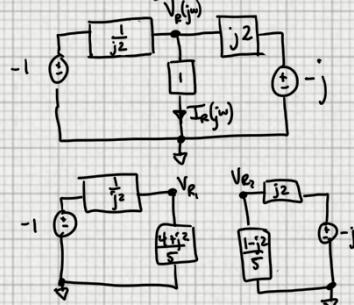

$$V_{R1} = -\frac{\frac{4\sqrt{2}}{5}}{\frac{1}{j\omega} + \frac{4\sqrt{2}}{5}} \quad V_{R2} = \frac{2+j}{1+j\omega}$$

$$V_{R1} = -\frac{\frac{4\sqrt{2}}{5}}{\frac{8-j}{10}} = -\frac{8+j4}{8-j} = -\frac{12+j8}{13}$$

$$V_{R2} = \frac{2-j}{13}$$

$$V_R = V_{R1} + V_{R2} = \frac{-12-j8+2-j3}{13} = \frac{-10-j11}{13}$$

$$|V_R| = \frac{\sqrt{221}}{13} \quad \angle V_R = \pi + \arctan\left(\frac{11}{10}\right)$$

$$\therefore V_R(t) = \frac{\sqrt{221}}{13} \cos(2t + \pi + \arctan(11/10))$$

$$P_R(t) = |V_R| |i_R| = \frac{221}{2 \cdot 13^2} = \frac{17}{26} = 0.6538$$

not sure what is going on

w/ multiple choice of

0.8

1.1


2.6

4.8

?

I have even done time domain and got the same answer


Given:

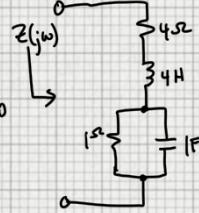

what frequency will resonate this ckt?

In other words, @ what f will $\text{Im}(Z(jw)) = 0$ or ∞

Let's transform into phasor:

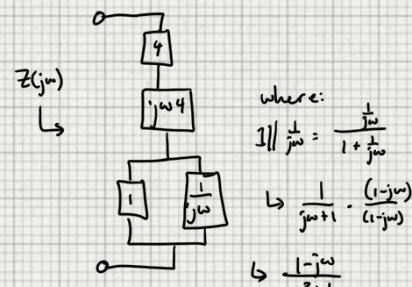

$$\therefore Z(jw) = 4 + jw4 + \frac{1-j\omega}{\omega^2+1}$$

$$(4 + \frac{1}{\omega^2+1}) + j(4\omega - \frac{\omega}{\omega^2+1})$$

$$\therefore \frac{\omega 4(\omega^2+1) - \omega}{\omega^2+1} = 0$$

$$\therefore (\omega^2+1) - \frac{1}{4} = 0$$

$$\therefore \omega^2 = -\frac{3}{4} \rightarrow \omega = j \pm \sqrt{\frac{3}{4}} = j\frac{\sqrt{3}}{2}$$

$$\therefore \omega = j\frac{\sqrt{3}}{2}$$


we see

$$Z(j\frac{\sqrt{3}}{2}) = 4(j\frac{\sqrt{3}}{2}) - \frac{j\frac{\sqrt{3}}{2}}{-\frac{3}{4}+1}$$


$$= j2\sqrt{3} - j\frac{\sqrt{3}}{4} - j2\sqrt{3} = 0$$

there is no real value of w that will yield a zero or ∞.

Therefore no resonant frequency.

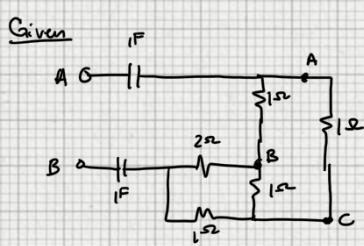


Using delta-wye transform

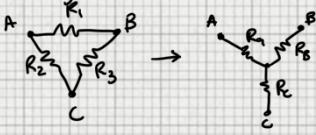


$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3} = \frac{1}{3}$$

$$R_b = \frac{R_1 R_3}{R_1 + R_2 + R_3} = \frac{1}{3}$$
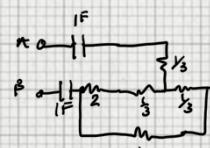
$$R_c = \frac{R_2 R_3}{R_1 + R_2 + R_3} = \frac{1}{3}$$


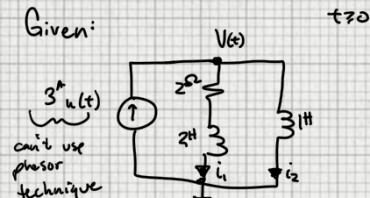
$$\frac{1}{s} F \xrightarrow{\frac{3}{33}} \frac{13}{11}$$



with no initial conditions
find $V(t)$. let's use laplace.

$$V(s) \xrightarrow{\text{transform}} \begin{array}{c} \frac{3}{s} u(t) \\ 1 \\ 2 \\ 3 \end{array}$$

where,
 $2(s+1) \parallel s$

$$\xrightarrow{\text{transform}} \frac{2s(s+1)}{2s+2+s} = \frac{2s(s+1)}{3s+2}$$

$$\therefore V(s) = \frac{2s(s+1)}{3s+2} \cdot \frac{3}{s} = \frac{6(s+1)}{3(s+\frac{2}{3})}$$

$$V(s) = \frac{2(s+1)}{s+\frac{2}{3}} = s \left(\frac{2}{s+\frac{2}{3}} \right) + \frac{2}{s+\frac{2}{3}}$$


$$\xrightarrow{\text{transform}} V(t) = \frac{d}{dt} \left(2e^{-\frac{2}{3}t} \right) + 2e^{-\frac{2}{3}t}$$

$$V(t) = -\frac{4}{3}e^{-\frac{2}{3}t} + \frac{6}{3}e^{-\frac{2}{3}t} = \frac{2}{3}e^{-\frac{2}{3}t}$$

$$\therefore V(t) = \frac{2}{3}e^{-\frac{2}{3}t} u(t) \quad \text{or}$$

$$\text{for } t \geq 0 \quad V(t) = \frac{2}{3}e^{-\frac{2}{3}t}$$

Given:

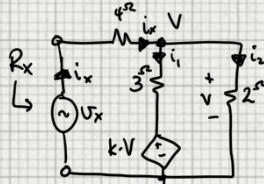

what value of k is needed
to make $R_x = 0$?

KCL

$$i_x = \frac{U_x - kV}{3} + \frac{V}{2} = \left(\frac{1-k}{3} + \frac{1}{2} \right) V$$

also

$$U_x - 4i_x = V$$

$$\therefore 6i_x = (2(1-k) + 3)V$$

$$\xrightarrow{\text{transform}} 6i_x = U_x - 4i_x \rightarrow \left(\frac{6}{S-2k} + \frac{4(S-2k)}{S-2k} \right) i_x = V$$

$$\frac{U_x}{i_x} = \frac{6+20-8k}{S-2k} = \frac{26-8k}{S-2k}$$

$$R_x = 0 \text{ when } 26-8k=0$$

$$\xrightarrow{\text{transform}} 13-4k=0 \rightarrow k = \frac{13}{4}$$

Checking

$$i_x = \frac{V(1-\frac{3}{4})}{3} + \frac{V}{2} = \left(-\frac{3}{4} + \frac{1}{2} \right) V = -\frac{V}{4}$$


$$V = -4i_x \quad \& \quad U_x = 4i_x + V = 4i_x - 4i_x$$

$$\& \quad \frac{U_x}{i_x} = 4-4=0 \quad \checkmark$$

Given



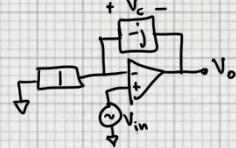where the sinusoidal steady state $\frac{V_o(t)}{V_{in}(t)}$ is equal to $\cos(\omega t)$,
what is the $V_c(t)$? ($\omega=1$)



\therefore using general negative feedback opamp equation

$$V_o = \left(\frac{z_1 + z_2}{z_1} \right) V_2 - \frac{z_2}{z_1} V_1^0$$

$$I = (1-j) V_{in}$$

$$\therefore V_{in} = \frac{1}{1-j} = \frac{1+j}{2}$$

$$V_c = V_{in} - V_o = \frac{1+j}{2} - 1 = -\frac{1+j}{2}$$

$$|V_c| = \frac{\sqrt{2}}{2} \quad \angle V_c = \arctan\left(\frac{-1}{1}\right) = -45^\circ$$

$$\therefore |V_c(t)| = \frac{\sqrt{2}}{2} \cos(t - 45^\circ)$$